
ELECTRONIC Basic NOTE

1. The evolution of a simple audio amplifier design, originally built with basic components, to a more powerful version suitable for driving loudspeakers:

The initial setup: using a Bipolar Junction Transistor (BJT), was limited in power output, prompting a switch to a TIP142 Darlington Transistor capable of handling higher current. However, this change introduced issues with audio clipping due to voltage drop constraints. Increasing the supply voltage to 12V improved performance, but overheating necessitated new resistor calculations and the addition of a heatsink.

Use of MOSFET: The IRFZ44N model is used, which offers lower resistance and potentially better efficiency. The video details the differences in operation between BJTs and MOSFETs, emphasizing **that MOSFETs require voltage control rather than current**. After adjustments, the MOSFET amplifier produced a louder output, but the creator notes that while it may seem superior, **BJTs typically provide better linear amplification and lower distortion**. The video concludes with a comparison of total harmonic distortion (THD) between the original sine wave, the Darlington amplifier, and the MOSFET amplifier, highlighting that while the **MOSFET design is simpler and louder, it may not be as efficient or distortion-free as the BJT design**.

2. the development of a haptic feedback breakout board using the BOS1921 piezo haptic driver IC, which is significantly cheaper than the development board:

designing a PCB based on the IC's datasheet: By designing a PCB based on the IC's datasheet, explore the I3C communication protocol, a successor to I2C was explored. After creating the schematic and PCB layout, the boards were assembled, but initial tests revealed issues due to incorrect capacitor orientation. Once corrected, the boards functioned properly, allowing for testing with a piezo actuator.

Advantages of I3C over I2C:

1. a higher data transfer rate (12.5MHz vs. 1MHz).
2. dynamic addressing.
3. support for Common Command Codes (CCC).

However, I3C's complexity requires compatible microcontrollers, which are currently limited. While I3C offers features like hot join and in-band interrupts, I2C remains sufficient for the haptic driver application, as evidenced by the original development board's use of

I2C. The creator was experimenting with a suitable microcontroller for I3C but concludes that I2C is likely adequate for their needs.

3. Saving Circuits from overvoltage:

Overvoltage events are rare but can instantly destroy electronic devices when they occur. Lightning strikes, grid switching, or electrostatic discharge (ESD) can cause overvoltage. Protective components are used to safeguard circuits from these events.

Protective Components

TVS Diode (Transient Voltage Suppressor)

- TVS Diode functions similarly to a regular diode and typically remains non-conductive at 5V stand-off voltage.
- At 6V, 1mA of current starts to flow, which rapidly increases with rising voltage.
- As a result, the TVS Diode clamps the voltage to around 10-12V and dissipates the excess energy as heat.
- TVS Diodes are often available in IC packages, making them easy to spot on a PCB.

MOV (Metal Oxide Varistor)

- MOV resembles a blue disk and rapidly decreases its resistance once the voltage exceeds a certain threshold.
- It dissipates excess voltage energy as heat and offers fast protection.
- MOVs are commonly used at the AC input of power supplies.
- MOVs are highly effective for handling high-energy surges.

GDT (Gas Discharge Tube)

- GDT is a tube-shaped component filled with inert gas.
- When overvoltage occurs, the gas ionizes, creating an arc that dissipates the energy as heat.
- GDTs respond slower compared to TVS Diodes but are ideal for high-voltage protection.

Ckt diagram:

4. Overvoltage Protection Components :

Overvoltage events are rare but can instantly destroy electronic devices when they occur. Causes include lightning strikes, grid switching, or electrostatic discharge (ESD). Protective components are essential to safeguarding circuits from these events.

Protective Components

TVS Diode (Transient Voltage Suppressor)

- TVS Diodes act like standard diodes under normal conditions, staying non-conductive at their specified stand-off voltage (e.g., 5V).
- When voltage exceeds this limit, current rapidly increases, clamping the voltage to around 10-12V while dissipating excess energy as heat.
- TVS Diodes are available in IC packages and are common on PCBs for circuit protection.

MOV (Metal Oxide Varistor)

- MOVs resemble blue disks and dramatically decrease their resistance when voltage surpasses a certain threshold.
- They dissipate excess voltage energy as heat, providing fast and effective protection.
- MOVs are frequently used at AC power supply inputs for robust surge protection.

GDT (Gas Discharge Tube)

- GDTs are tube-shaped components filled with inert gas.
- When voltage spikes, the gas ionizes, forming an arc that dissipates energy as heat.
- While GDTs respond slower than TVS Diodes, they excel in high-voltage protection scenarios.

Circuit Analysis and Function:

- TVS Diodes are typically placed between voltage pins and ground in circuits.
- MOVs are connected across power lines, often with a thermal fuse that disconnects under high current conditions.
- Testing with a 15,000V overvoltage source showed that TVS Diodes and MOVs successfully protected the test circuit.
- The GDT was unsuitable for protecting the 5V microcontroller circuit due to its higher voltage protection threshold.

4. Key Differences and Practical Insights

- **TVS Diode:** Fast response, effective for low-energy transients.
- **MOV:** Effective at handling high-energy surges, ideal for power supply circuits.
- **GDT:** Provides robust protection for extreme voltage spikes but responds slower.

5. ELECTRICAL GROUNDING AND PROTECTION SYSTEM :

1. COMPONENT WORKING PRINCIPLE

SOIL AS A CONDUCTOR

- **SOIL CAN CONDUCT ELECTRICITY, THOUGH ITS CONDUCTIVITY VARIES BASED ON MOISTURE CONTENT AND MINERAL COMPOSITION.**
- **LARGER METAL PLATES IMPROVE CONDUCTIVITY BY INCREASING SURFACE AREA IN CONTACT WITH THE SOIL.**

PROTECTIVE EARTH (PE) WIRE

- **FOUND IN AC POWER CABLES, TYPICALLY MARKED WITH GREEN-YELLOW INSULATION.**
- **PE WIRE CONNECTS THE METAL CHASSIS OF APPLIANCES TO THE GROUND, PROVIDING A SAFE PATH FOR FAULT CURRENT.**
- **THIS ENSURES THAT IF THE LIVE WIRE TOUCHES THE METAL CASING, THE CURRENT FLOWS THROUGH THE PE WIRE INSTEAD OF THE USER, TRIGGERING SAFETY DEVICES.**

CIRCUIT BREAKER (CB)

- **CUTS OFF POWER DURING HIGH CURRENT SURGES CAUSED BY FAULTS LIKE SHORT CIRCUITS.**
- **ACTIVATES WHEN CURRENT EXCEEDS ITS RATED LIMIT.**

RESIDUAL CURRENT BREAKER (RCB)

- **MONITORS THE DIFFERENCE BETWEEN LIVE AND NEUTRAL CURRENT.**
- **TRIPS WHEN THERE'S AN IMBALANCE, OFTEN CAUSED BY CURRENT LEAKAGE TO GROUND, PROVIDING ENHANCED SAFETY.**

2. CIRCUIT DIAGRAM AND FUNCTION ANALYSIS

- **POWER FLOW:**
 - **LIVE WIRE (L1): SUPPLIES THE MAIN VOLTAGE (230V IN GERMANY).**
 - **NEUTRAL WIRE (N): COMPLETES THE CIRCUIT BY RETURNING CURRENT.**
 - **PROTECTIVE EARTH (PE): ACTS AS A SAFETY PATH FOR EXCESS CURRENT TO FLOW DIRECTLY TO THE GROUND IN CASE OF FAULTS.**
- **TOASTER DEMONSTRATION:**
 - **LIVE AND NEUTRAL WIRES POWER THE RESISTIVE HEATING ELEMENT INSIDE THE TOASTER.**
 - **THE PE WIRE CONNECTS TO THE METAL HOUSING OF THE TOASTER FOR SAFETY.**
- **FAULT SIMULATION:**
 - **IF THE LIVE WIRE ACCIDENTALLY CONTACTS THE METAL CHASSIS, THE CURRENT FLOWS THROUGH THE PE WIRE, CREATING A SHORT CIRCUIT.**

- THIS ACTION TRIGGERS BOTH THE CIRCUIT BREAKER AND THE **RCB**, CUTTING OFF POWER TO PREVENT ELECTRIC SHOCK.
- **EARTH ROD:**
 - A THICK METAL ROD BURIED DEEP INTO THE EARTH (SOMETIMES UP TO 9 METERS) HELPS DISSIPATE STATIC CHARGES AND FAULT CURRENTS SAFELY.

3. CORE CONCEPTS FROM THE VIDEO

- **EARTH'S ROLE IN ELECTRICAL SYSTEMS:**
 - THE EARTH SERVES AS A MASSIVE REFERENCE POTENTIAL AT **0V**, ENSURING STABLE VOLTAGE LEVELS IN SYSTEMS.
 - IT ABSORBS EXCESS ELECTRONS DURING STATIC DISCHARGES, LIGHTNING STRIKES, OR SUDDEN VOLTAGE SPIKES.
- **STATIC ELECTRICITY PROTECTION:**
 - GROUNDING PREVENTS HAZARDOUS ELECTROSTATIC BUILDUP, CRUCIAL IN ENVIRONMENTS LIKE SOLAR PANEL INSTALLATIONS OR ELECTRONICS ASSEMBLY AREAS.
- **SCHEMATIC DESIGN IN PCBs:**
 - IN **PCB** DESIGNS, THE BOTTOM LAYER OFTEN ACTS AS A CONTINUOUS GROUND PLANE TO ENSURE NOISE REDUCTION, IMPROVED SIGNAL INTEGRITY, AND EFFECTIVE GROUNDING FOR COMPONENTS.

4. KEY TAKEAWAYS FOR UNDERSTANDING

- GROUNDING'S PRIMARY ROLE IS USER PROTECTION BY PROVIDING A SAFE PATH FOR EXCESS CURRENT TO FLOW.
- EARTH ITSELF CAN CONDUCT ELECTRICITY AND SERVES AS A STABLE REFERENCE VOLTAGE.
- **RCB** AND CIRCUIT BREAKERS WORK TOGETHER TO SAFEGUARD APPLIANCES AND INDIVIDUALS.
- IN **PCB** DESIGNS, THE "GROUND" SYMBOL TYPICALLY REPRESENTS A COMMON REFERENCE POTENTIAL, NOT ALWAYS PHYSICALLY CONNECTED TO THE EARTH.

5. RECOMMENDED NEXT STEPS FOR DEEP UNDERSTANDING

- STUDY THE DATASHEETS OF KEY COMPONENTS LIKE **RCBs**, **CBs**, AND **PE WIRES**.
- DRAW THE CIRCUIT DIAGRAM DEMONSTRATED IN THE VIDEO, ENSURING TO ILLUSTRATE THE **PE** WIRE CONNECTION POINTS AND FAULT PROTECTION MECHANISMS.
- RESEARCH GROUNDING METHODS IN VARIOUS ELECTRICAL SYSTEMS SUCH AS SOLAR INSTALLATIONS, POWER GRIDS, AND HOME APPLIANCES.

6. Power Inductors :

Power inductors are key components in electronics, especially in power supply circuits. Identifying them is relatively easy since they typically consist of copper wire wound around a ferromagnetic core. There are various types:

- **Conventional Power Inductors:** Found in larger power supplies.
- **Surface Mount Device (SMD) Inductors:** Compact and commonly seen in smaller power supplies.
- **Color Ring Inductors:** Resemble resistors but are inductors marked with color bands for easy identification.

Color Ring Inductors: Characteristics and Limitations

- **Advantages:** Affordable, widely available, and easy to identify.
- **Disadvantages:** Lack detailed datasheets, making it difficult to determine their full electrical properties. For example, they often lack information about saturation current, which is crucial for power applications.

Experiment: Boost Converter Test

A boost converter was tested to compare the performance of a standard 22uH inductor with a 22uH color ring inductor.

- **Original Inductor Performance:** Handled 1A of current before voltage started to degrade.
- **Color Ring Inductor Performance:** Managed only 0.5A before voltage breakdown and increased noise.

Conclusion: Despite having the same inductance value (22uH), the color ring inductor could handle significantly less current due to a lower saturation current rating.

Measuring Saturation Current

Since LCR meters cannot measure saturation current directly, a custom test circuit was built:

- **Circuit Components:**
 - A MOSFET controlled by a function generator to allow brief current pulses.

- A small resistor to measure voltage changes (since current = voltage/resistance).
- **Test Results:**
 - **Original Inductor:** Saturation at 4A (400mV reading).
 - **Color Ring Inductor:** Saturation at 1.6A (160mV reading).

5. Why Saturation Current Matters

- **Inductor's Energy Storage Formula:** $\text{Energy} = (\text{Inductance}/2) \times \text{Current}^2$
- When the saturation current is exceeded, the inductor behaves like a resistor, posing a risk to the circuit and the component itself.
- Heat further reduces the saturation current, making the situation worse under heavy loads.

Practical Applications and Recommendations

- **Color Ring Inductors** are suitable for low-power applications like:
 - Signal filtering
 - Oscillators
 - Experimental electronics for beginners
- They are **not recommended** for high-power circuits or power supplies where current capacity is critical.

While color ring inductors have their place in electronics, they must be used within their limitations. They are ideal for low-power circuits but should be avoided in power-heavy applications unless their specifications are confirmed. Understanding their limitations can help beginners experiment safely and affordably.

7. Power Inductors:

Power inductors are key components in electronics, especially in power supply circuits. Identifying them is relatively easy since they typically consist of copper wire wound around a ferromagnetic core. There are various types:

- **Conventional Power Inductors:** Found in larger power supplies.

- **Surface Mount Device (SMD) Inductors:** Compact and commonly seen in smaller power supplies.
- **Color Ring Inductors:** Resemble resistors but are inductors marked with color bands for easy identification.

Color Ring Inductors: Characteristics and Limitations

- **Advantages:** Affordable, widely available, and easy to identify.
- **Disadvantages:** Lack detailed datasheets, making it difficult to determine their full electrical properties. For example, they often lack information about saturation current, which is crucial for power applications.

Experiment: Boost Converter Test

A boost converter was tested to compare the performance of a standard 22uH inductor with a 22uH color ring inductor.

- **Original Inductor Performance:** Handled 1A of current before voltage started to degrade.
- **Color Ring Inductor Performance:** Managed only 0.5A before voltage breakdown and increased noise.

Conclusion: Despite having the same inductance value (22uH), the color ring inductor could handle significantly less current due to a lower saturation current rating.

Measuring Saturation Current

Since LCR meters cannot measure saturation current directly, a custom test circuit was built:

- **Circuit Components:**
 - A MOSFET controlled by a function generator to allow brief current pulses.
 - A small resistor to measure voltage changes (since current = voltage/resistance).
- **Test Results:**
 - **Original Inductor:** Saturation at 4A (400mV reading).
 - **Color Ring Inductor:** Saturation at 1.6A (160mV reading).

Why Saturation Current Matters:

- **Inductor's Energy Storage Formula:** $\text{Energy} = (\text{Inductance}/2) \times \text{Current}^2$
- When the saturation current is exceeded, the inductor behaves like a resistor, posing a risk to the circuit and the component itself.
- Heat further reduces the saturation current, making the situation worse under heavy loads.

Practical Applications and Recommendations:

- **Color Ring Inductors** are suitable for low-power applications like:
 - Signal filtering
 - Oscillators
 - Experimental electronics for beginners
- They are **not recommended** for high-power circuits or power supplies where current capacity is critical.

While color ring inductors have their place in electronics, they must be used within their limitations. They are ideal for low-power circuits but should be avoided in power-heavy applications unless their specifications are confirmed. Understanding their limitations can help beginners experiment safely and affordably.

8. RESETTABLE FUSE (PPTC) WORKING PRINCIPLE AND CIRCUIT EXPLANATION

1. WORKING PRINCIPLE OF THE PPTC (POLYMERIC POSITIVE TEMPERATURE COEFFICIENT) DEVICE

- **A PPTC DEVICE BEHAVES LIKE A VARIABLE RESISTOR WHOSE RESISTANCE INCREASES SHARPLY WHEN EXPOSED TO EXCESSIVE CURRENT.**
- **WHEN OVERCURRENT FLOWS, THE PPTC HEATS UP. AS ITS TEMPERATURE RISES, ITS RESISTANCE INCREASES SIGNIFICANTLY, RESTRICTING THE CURRENT FLOW TO A MINIMAL "LEAKAGE CURRENT."**
- **UNLIKE TRADITIONAL GLASS FUSES, PPTCs ARE RESETTABLE. WHEN THE TEMPERATURE DECREASES, THEIR RESISTANCE DROPS BACK TO NORMAL, RESTORING THE CIRCUIT.**

2. ROLE OF PPTC IN THE CIRCUIT

- **THE PPTC IS PLACED IN SERIES WITH THE LOAD (E.G., LED STRIP OR POWER CIRCUIT) TO PROTECT IT FROM OVERCURRENT SITUATIONS.**
- **DURING NORMAL OPERATION, THE PPTC OFFERS MINIMAL RESISTANCE AND ALLOWS CURRENT TO FLOW UNINTERRUPTED.**
- **IF EXCESSIVE CURRENT OCCURS (E.G., 1A IN THE DEMONSTRATED CIRCUIT), THE PPTC HEATS UP, INCREASES ITS RESISTANCE, AND LIMITS THE CURRENT TO A SAFER LEAKAGE CURRENT (ABOUT 103mA IN THE DEMO).**

3. CIRCUIT DIAGRAM AND COMPONENT EXPLANATION

- **POWER SOURCE: PROVIDES 12V FOR THE LED STRIP OR TEST CIRCUIT.**
- **PPTC FUSE: RATED FOR 0.5A HOLD CURRENT AND 1A TRIP CURRENT IN THE INITIAL EXAMPLE. THIS ENSURES THE FUSE WON'T TRIP DURING NORMAL USAGE BUT WILL ACTIVATE UNDER EXCESSIVE LOAD.**
- **LOAD (LED STRIP/POWER RESISTOR): THE PRIMARY COMPONENT PROTECTED BY THE PPTC.**
- **TRIP INDICATOR: CONSISTS OF THREE PARALLEL COMPONENTS THAT LIGHT UP WHEN THE PPTC ENTERS ITS HIGH-RESISTANCE STATE, SERVING AS A VISUAL INDICATOR.**

4. KEY INSIGHTS FROM THE VIDEO

- **CHOOSING THE RIGHT PPTC:**
 - **MAXIMUM VOLTAGE/CURRENT: ENSURE THESE RATINGS EXCEED THE CIRCUIT'S OPERATIONAL VALUES.**
 - **HOLD CURRENT: SELECT A FUSE THAT COMFORTABLY HANDLES YOUR DEVICE'S STANDARD CURRENT.**
 - **TRIP CURRENT: SELECT A VALUE JUST ABOVE YOUR MAXIMUM EXPECTED LOAD TO ENSURE RELIABLE PROTECTION.**
- **PPTC LIMITATIONS:**
 - **PPTCs ARE SLOWER THAN ELECTRONIC SOLUTIONS LIKE eFUSES BUT OFTEN FASTER THAN TRADITIONAL GLASS FUSES.**
 - **PPTCs NEVER CUT THE CURRENT TO ZERO, MAINTAINING A LOW LEAKAGE CURRENT WHEN TRIPPED.**
- **APPLICATION EXAMPLES:**

- **PPTCs ARE COMMONLY USED IN BATTERY PACKS, LED STRIPS, AND DEVICES LIKE THE RASPBERRY PI.**
- **ALTERNATIVE SOLUTIONS:**
 - **GLASS FUSES: RELIABLE BUT REQUIRE MANUAL REPLACEMENT.**
 - **EFUSES: FASTER, MORE PRECISE, AND EFFICIENT BUT REQUIRE MORE COMPLEX SETUP AND ARE NON-RESETTABLE.**

5. PRACTICAL RECOMMENDATIONS

- **CAREFULLY ANALYZE THE CURRENT DRAW AND ENVIRONMENT WHERE THE PPTC WILL OPERATE TO ENSURE OPTIMAL PERFORMANCE.**
- **UNDERSTAND THAT PPTCs MAY TAKE LONGER TO RESET TO THEIR ORIGINAL RESISTANCE VALUE AFTER TRIPPING.**
- **FOR CRITICAL SYSTEMS WITH STRICT SAFETY DEMANDS, COMBINING DIFFERENT PROTECTION METHODS MAY BE IDEAL.**

9. RESETTABLE FUSE AND LATCH CIRCUIT NOTES

RESETTABLE FUSE (PPTC) WORKING PRINCIPLE

- **POLYMERIC POSITIVE TEMPERATURE COEFFICIENT (PPTC): THESE DEVICES INCREASE THEIR RESISTANCE WHEN THEIR TEMPERATURE RISES, PROTECTING CIRCUITS FROM OVERCURRENT CONDITIONS.**
- **WHEN CURRENT EXCEEDS THE TRIP THRESHOLD, THE PPTC'S RESISTANCE RISES SHARPLY, LIMITING CURRENT FLOW. IT REMAINS IN THIS HIGH-RESISTANCE STATE UNTIL POWER IS REMOVED AND THE DEVICE COOLS DOWN.**
- **UNLIKE TRADITIONAL GLASS FUSES, PPTCs AUTOMATICALLY RESET AFTER COOLING, MAKING THEM REUSABLE.**

KEY PARAMETERS OF PPTCs

- **MAXIMUM VOLTAGE & CURRENT: EXCEEDING THESE CAN DAMAGE THE FUSE.**
- **HOLD CURRENT: MAXIMUM CURRENT THAT CAN FLOW WITHOUT THE FUSE TRIPPING.**
- **TRIP CURRENT: CURRENT THAT TRIGGERS THE PPTC INTO ITS HIGH-RESISTANCE STATE.**

PRACTICAL INSIGHTS

- **PPTCs ARE SLOWER THAN TRADITIONAL FUSES BUT ARE MORE CONVENIENT FOR REPEATED USE.**
- **THEY DO NOT CUT OFF CURRENT ENTIRELY; INSTEAD, THEY REDUCE IT TO A SAFER LEVEL TO PREVENT DAMAGE.**
- **THEY ARE COMMON IN BATTERY PROTECTION CIRCUITS, LED STRIPS, AND OTHER APPLICATIONS WHERE AUTOMATED RESET IS USEFUL.**

LATCH CIRCUIT WORKING PRINCIPLE

- **DEFINITION: A LATCH CIRCUIT CONTROLS A SWITCHING ELEMENT'S STATE BASED ON SET AND RESET SIGNALS, REQUIRING ONLY A PULSE TO TOGGLE.**
- **SR LATCH IC (74LS279): FEATURES SET (S) AND RESET (R) INPUTS WITH Q AS THE OUTPUT.**
 - **APPLYING A HIGH VOLTAGE PULSE TO SET LATCHES THE OUTPUT HIGH.**
 - **APPLYING A HIGH VOLTAGE PULSE TO RESET TURNS THE OUTPUT LOW.**

NOR GATE-BASED LATCH

- **CONSISTS OF TWO NOR GATES CONNECTED TO EACH OTHER:**
 - **NOR GATES OUTPUT A HIGH SIGNAL ONLY WHEN BOTH INPUTS ARE LOW.**
 - **THIS SIMPLE DESIGN ACHIEVES SR LATCH FUNCTIONALITY USING BASIC LOGIC GATES.**

TRANSISTOR-BASED LATCH

- **USES BJTs, MOSFETs, AND CAPACITORS FOR MORE CONTROL AND HIGHER CURRENT HANDLING.**
- **EXAMPLE CIRCUIT PROCESS:**
 1. **THE MOSFET GATE IS TIED HIGH (KEEPING IT OFF) UNTIL THE SET BUTTON IS PRESSED.**
 2. **THE LEFT BJT ACTIVATES, PULLING THE MOSFET GATE LOW TO TURN IT ON.**
 3. **THE RIGHT BJT, COMBINED WITH A CAPACITOR, CONTROLS THE TIMING AND PREVENTS RAPID RESET.**

APPLICATIONS

- **LIGHTING SYSTEMS: SEMICONDUCTOR-BASED LATCHES REDUCE COST COMPARED TO MECHANICAL TOGGLE SWITCHES IN HIGH-CURRENT APPLICATIONS.**
- **MICROCONTROLLER POWER CONTROL: A LATCH CAN ALLOW THE CONTROLLER TO POWER ITSELF OFF AUTOMATICALLY.**
- **OVERCURRENT PROTECTION CIRCUITS: OFTEN USE RELAYS OR LATCHES TO MAINTAIN A STABLE SHUTDOWN STATE AFTER A FAULT IS DETECTED.**

CONCLUSION

- **PPTCs ARE EFFECTIVE FOR OVERCURRENT PROTECTION BUT MAY REQUIRE COMPLEMENTARY COMPONENTS LIKE LATCHES FOR COMPLETE CIRCUIT STABILITY.**
- **LATCH CIRCUITS ARE VERSATILE AND USEFUL FOR POWER CONTROL, FAULT PROTECTION, AND AUTOMATED SHUTDOWN DESIGNS. UNDERSTANDING LOGIC GATE BEHAVIOR AND TRANSISTOR OPERATION IS KEY TO MASTERING THESE CIRCUITS.**

10. THE DISCUSSION BEGINS WITH THE COMMONALITY OF BATTERIES AND POWER SUPPLIES, PRIMARILY THEIR DC OUTPUT VOLTAGE, WHICH POWERS MOST ELECTRONIC DEVICES. HOWEVER, EXCEPTIONS EXIST, SUCH AS WAVEFORM GENERATORS THAT CAN PRODUCE BOTH POSITIVE AND NEGATIVE VOLTAGES, ESSENTIAL FOR VARIOUS APPLICATIONS LIKE AUDIO AMPLIFIERS AND SENSORS. THE VIDEO AIMS TO DEMONSTRATE METHODS FOR CREATING DUAL RAIL VOLTAGE SUPPLIES.

STARTING WITH SIMPLE BOARDS THAT CAN BE ORDERED ONLINE, THE OUTPUT CAN PROVIDE +12V AND -12V FROM A 5V INPUT. ADDITIONALLY, A STANDARD BOOST CONVERTER CAN BE MODIFIED TO CREATE DUAL RAIL VOLTAGE USING AN INVERTING CHARGE PUMP, WHICH GENERATES NEGATIVE VOLTAGE BY CHARGING CAPACITORS IN A SPECIFIC MANNER.

DESPITE THE SIMPLICITY, THESE CIRCUITS OFTEN FACE LIMITATIONS IN OUTPUT CURRENT AND NOISE, WHICH CAN AFFECT SENSITIVE APPLICATIONS. A MORE ROBUST SOLUTION INVOLVES USING A CENTER-TAPPED TRANSFORMER, WHICH CAN PROVIDE STABLE DUAL RAIL OUTPUTS WITHOUT SIGNIFICANT NOISE.

ALTERNATIVELY, A VOLTAGE DIVIDER CAN CREATE VIRTUAL GROUND, BUT IT STRUGGLES WITH CURRENT STABILITY. AN OPERATIONAL AMPLIFIER CAN BUFFER THIS SETUP, STABILIZING THE VIRTUAL GROUND AND ALLOWING FOR MORE CURRENT DRAW.

FURTHER METHODS INCLUDE USING SPECIFIC ICs OR DISCRETE TRANSISTOR SOLUTIONS FOR VOLTAGE RAIL SPLITTING. THE VIDEO CONCLUDES BY EQUIPPING VIEWERS WITH KNOWLEDGE ABOUT VARIOUS DUAL RAIL POWER SUPPLIES AND THEIR APPLICATIONS, ENCOURAGING EXPLORATION OF ADDITIONAL RESOURCES FOR DEEPER UNDERSTANDING.

11. DIGITAL POTENTIOMETERS AND THEIR WORKING PRINCIPLE

OVERVIEW OF THE VIDEO CONCEPT:

THE VIDEO INTRODUCES THE CONCEPT OF DIGITAL POTENTIOMETERS AS A MODERN, DIGITALLY CONTROLLED ALTERNATIVE TO TRADITIONAL MECHANICAL POTENTIOMETERS. THESE DEVICES ARE PARTICULARLY USEFUL FOR APPLICATIONS WHERE A MICROCONTROLLER NEEDS TO ADJUST RESISTANCE LEVELS, SUCH AS DIMMING LEDs OR MODIFYING THE THRESHOLD VALUE FOR SENSORS, WITHOUT MANUAL INTERVENTION. THE VIDEO WALKS THROUGH THE COMPONENTS AND THEIR WORKING PRINCIPLES, HOW TO INTERFACE THEM WITH A MICROCONTROLLER, AND ADDRESSES PRACTICAL ISSUES SUCH AS VOLTAGE LIMITATIONS.

WORKING PRINCIPLE OF DIGITAL POTENTIOMETER (ICs LIKE X9C103 AND X9C104)

DIGITAL POTENTIOMETER FUNCTIONALITY:

1. CORE MECHANISM:

- A DIGITAL POTENTIOMETER WORKS BY USING A SET OF INTERNAL RESISTORS (99 IN THE X9C103) BETWEEN AN UPPER AND LOWER TERMINAL. THE WIPER CAN BE POSITIONED TO CREATE ADJUSTABLE RESISTANCE, JUST LIKE IN MECHANICAL POTENTIOMETERS.
- THE POSITION OF THE WIPER IS CONTROLLED BY DIGITAL INPUTS RATHER THAN MANUALLY ROTATING A KNOB.

2. ADJUSTMENT:

- THE WIPER CAN BE MOVED EITHER TOWARDS THE UPPER OR LOWER TERMINAL, ALTERING THE RESISTANCE IN THE CIRCUIT.
- THE IC PROVIDES AN ADJUSTABLE VOLTAGE DIVIDER, WHICH IS KEY TO VARYING RESISTANCE IN CIRCUITS WHERE VOLTAGE NEEDS TO BE MODIFIED.

3. CONTROL MECHANISM:

- THE WIPER IS MOVED BY SENDING SPECIFIC SIGNALS TO THE IC'S PINS. IN THE CASE OF THE X9C103, THREE DIGITAL INPUTS—UP, DOWN, AND CHIP SELECT—ARE USED TO INCREMENT OR DECREMENT THE WIPER POSITION:
 - UP AND DOWN PINS DETERMINE THE DIRECTION OF THE MOVEMENT (UP OR DOWN).
 - THE CHIP SELECT PIN IS USED TO STORE THE WIPER'S POSITION IN MEMORY, ENSURING THAT THE SETTING PERSISTS AFTER POWER-OFF.
 - THE INCREMENT PIN PULLS THE WIPER BY ONE STEP FOR EACH ACTIVATION.

4. RESOLUTION:

- THE DIGITAL POTENTIOMETER PROVIDES A FIXED RESOLUTION OF 100 STEPS FOR ADJUSTING RESISTANCE (E.G., FROM 0V TO 5V WITH A GRANULARITY OF 1/100TH OF THE TOTAL RANGE). WHILE THIS RESOLUTION IS ADEQUATE FOR MANY APPLICATIONS, IT MAY BE NOTICEABLE IN CERTAIN SENSITIVE SETUPS.

CIRCUIT DESIGN AND FUNCTIONALITY

CIRCUIT COMPONENTS:

1. IC PINOUT:

- THE IC CONSISTS OF 3 DIGITAL INPUT PINS, A VCC PIN (5V SUPPLY), AND GND.
- THE UPPER AND LOWER TERMINALS OF THE DIGITAL POTENTIOMETER ARE CONNECTED TO THE POWER SUPPLY AND GROUND, RESPECTIVELY, CREATING A VARIABLE VOLTAGE DIVIDER.

2. INTEGRATION WITH MICROCONTROLLER:

- IN A TYPICAL SETUP, THE MICROCONTROLLER SENDS SIGNALS THROUGH PUSH BUTTONS (CONNECTED TO THE 3 DIGITAL INPUTS) TO CONTROL THE WIPER'S POSITION AND THUS ADJUST THE RESISTANCE.
- THE MICROCONTROLLER MAY ALSO INTERACT WITH REAL-TIME CLOCKS (RTCs) TO ADJUST PARAMETERS LIKE LED BRIGHTNESS BASED ON TIME OF DAY, THEREBY INTEGRATING TIME-BASED CONTROL INTO THE CIRCUIT.

3. PRACTICAL APPLICATION EXAMPLE:

- THE VIDEO DEMONSTRATES HOW THE DIGITAL POTENTIOMETER CAN BE USED TO CONTROL THE BRIGHTNESS OF A HIGH-POWER **LED** DRIVEN BY A BOOST CONVERTER.
- THE MICROCONTROLLER ADJUSTS THE POTENTIOMETER DIGITALLY TO DIM THE **LED** BY CHANGING THE VOLTAGE SUPPLIED TO THE **LED**, SIMULATING THE ADJUSTMENT THAT WOULD OTHERWISE BE DONE WITH A MECHANICAL POTENTIOMETER.

12. TL431: Working Principle & Applications

Working Principle:

- **TL431** is a **Precision Programmable Reference IC** with a built-in 2.495V reference.
- It compares the reference voltage (Ref pin) to the internal reference. If the Ref voltage exceeds 2.495V, the internal transistor turns on, pulling the output low. If below, the output stays high.
- Used as an **adjustable zener diode** with a voltage divider.

Applications:

1. **Adjustable Zener Diode:** Custom voltage references (e.g., 5V using resistors).
2. **Voltage Monitoring & Feedback:** Used in feedback circuits for **power supplies** and **battery protection**.
3. **Constant Current Sink:** For precision current regulation.

In Switched-Mode Power Supplies (SMPS):

- **Feedback control:** Maintains stable voltage by adjusting PWM duty cycle.
- **Components:** Voltage divider, **optocoupler**, and **resistors** for voltage setting and feedback.

TL431 is essential for efficient, stable voltage regulation in power supplies.

13. Oscilloscope Basics

Why Use an Oscilloscope:

It visualizes voltage or current over time, essential for analyzing waveforms in circuits.

Choosing an Oscilloscope:

- **Channels:** 4 channels are ideal.
- **Bandwidth:** Pick a scope with at least 5x the highest frequency of your signal.

- **Sampling Rate:** 2GSa/s is sufficient for most tasks.

Using Probes:

- Attach probes to the circuit and ground.
- **Scaling factor:** x1 (no scaling) or x10 (better bandwidth).

Settings:

- **Triggering:** Syncs the oscilloscope with the signal for stable display.
- Adjust **vertical** and **horizontal divisions** for proper scaling.
- Use built-in tools to measure frequency and rise time.

Advanced Features:

- **Ripple Measurement:** Use AC coupling to measure voltage fluctuations.
- **Current Measurement:** Use current shunt/clamp for accurate readings.

Mains Voltage Safety:

- Use **10:1 scaling** for high voltage measurements.
- **Differential probes** prevent damage when measuring mains voltage.

14. Using eFuse IC for Circuit Protection

- **Powering Your Circuit:**

A USB port is a simple and effective way to power your circuit via power banks (5V). It ensures portability and built-in protection features like short-circuit and reverse voltage prevention.

- **eFuse IC for Protection:**

For projects using external power sources (batteries, solar panels, etc.), an **eFuse IC** is essential to protect against:

- **Undervoltage**
- **Overvoltage**
- **Reverse Voltage** (requires additional protection)
- **Overcurrent**

- **Example IC (TPS259621):**

- Operates between 2.7V to 19V.

- Features adjustable current limits (0.125A to 2A).
- Built-in undervoltage and overvoltage protection.
- **Circuit Setup:**
 - **IN, OUT, and GND** pins connect straightforwardly.
 - **Undervoltage Protection:** Achieved by pulling the Enable/Undervoltage pin with a resistor, activating the circuit above 4.5V and cutting power below 4V.
 - **Overvoltage Protection:** A resistor (470kΩ) clamps the output voltage to 5.35V when it exceeds the limit.
 - **Current Limiting:** A resistor on the Current Limiting Pin sets the current to 200mA.
- **Additional Features:**
 - **Overtemperature Protection** halts the circuit if it gets too hot.
 - **Reverse Voltage Protection** can be added with a **P-Channel MOSFET**.
- **Advanced eFuse ICs:**
Some more advanced eFuse ICs come with built-in reverse voltage protection but are harder to hand-solder.

15. EXPLORING TUBE AMPLIFIERS

- **TUBE AMPLIFIERS OVERVIEW:**
 - **VACUUM TUBES (INVENTED IN 1906) WERE REPLACED BY TRANSISTORS, BUT STILL USED IN MODERN TUBE AMPS.**
 - **TRIODE TUBES (E.G., 6J4) AMPLIFY AUDIO BUT DON'T DIRECTLY POWER SPEAKERS—THEY SERVE AS PRE-AMPLIFIERS WHILE OTHER AMPLIFIER TYPES PROVIDE THE REAL POWER AMPLIFICATION.**
- **WHY TUBE AMPLIFIERS?**
 - **SOUND QUALITY: TUBE AMPS ARE KNOWN FOR PROVIDING A "WARM" OR "NATURAL" SOUND. THE DISTORTIONS THEY ADD ARE CONSIDERED PLEASANT BY MANY.**
 - **HOW TUBES WORK: A LOW-POWER CONTROL SIGNAL ON THE GRID CONTROLS CURRENT FLOW BETWEEN THE CATHODE AND ANODE, AMPLIFYING THE SIGNAL.**

- **CONSTRUCTION PROCESS:**
 - TO POWER A TUBE, **6.3V** IS APPLIED TO THE HEATER PINS, WHICH HEAT UP AND EXCITE THE ELECTRONS.
 - THE CONTROL SIGNAL APPLIED TO THE GRID ADJUSTS THE CURRENT FLOW.
 - TUBES REQUIRE HIGH **DC** VOLTAGE (**~100V**) TO FUNCTION, WHICH IS RISKY FOR BEGINNERS.
 - **TUBE AMPLIFIER DESIGN:**
 - THE PURCHASED TUBE AMPLIFIER USES CLASS **D** AMPLIFIERS FOR SPEAKER OUTPUT AND A HEADPHONE AMPLIFIER FOR THE HEADPHONE OUTPUT, WHILE TUBES ONLY PRE-AMPLIFY.
 - COMPARED TO TRANSISTORS, TUBES HAVE MORE DISTORTION BUT ARE LIKED FOR THEIR PLEASANT SOUND CHARACTERISTICS.
 - **CLASS A AMPLIFIER EXAMPLE:**
 - BOTH VACUUM TUBE AND TRANSISTOR (**BJT**) CIRCUITS ARE BUILT TO COMPARE PERFORMANCE.
 - THE WAVEFORM FROM BOTH AMPLIFIERS IS SIMILAR, BUT TUBES GENERATE MORE DISTORTION DUE TO THEIR LESS LINEAR BEHAVIOR.
 - **ADVANTAGES OF TUBE AMPS:**
 - LESS DISTORTION FROM OVERDRIVE (TUBES DON'T CLIP LIKE TRANSISTORS).
 - LOWER HIGH-FREQUENCY HARMONICS, WHICH SOME PEOPLE PREFER.
 - **CONCLUSION:**
 - TUBES ADD PLEASING DISTORTIONS THAT SOME AUDIOPHILES PREFER, BUT THEY ARE NOT THE BEST CHOICE FOR EVERYONE.
 - **DISADVANTAGES:** THEY REQUIRE HIGH VOLTAGE, PRODUCE HEAT, AND ARE LESS EFFICIENT THAN SOLID-STATE OPTIONS.
-

16. ASYNCHRONOUS (INDUCTION) MOTORS

- **OVERVIEW:** WIDELY USED IN INDUSTRY FOR THEIR SIMPLICITY AND DURABILITY, THESE MOTORS RUN ON 3-PHASE AC VOLTAGE AND DON'T NEED MAGNETS LIKE BLDC MOTORS.
- **WORKING:** A ROTATING MAGNETIC FIELD IN THE STATOR INDUCES CURRENT IN THE ROTOR, CAUSING IT TO SPIN SLIGHTLY SLOWER THAN THE STATOR'S FIELD (CALLED "SLIP").
- **SPEED CONTROL:** SPEED CAN BE ADJUSTED WITH MOTORS HAVING MORE POLES OR ELECTRONIC FREQUENCY CONVERTERS.
- **SINGLE-PHASE USE:** SMALLER MOTORS MAY USE A CAPACITOR TO SIMULATE 3-PHASE POWER.
- **ADVANTAGES:** SIMPLE, RELIABLE, CHEAP, AND DON'T REQUIRE DC VOLTAGE OR COMPLEX DRIVERS.

17. I2S AUDIO WITH ESP32

- **OVERVIEW:** USING ESP32 TO RECORD AND PLAYBACK AUDIO, WE USE I2S (INTER-IC SOUND) FOR EFFICIENT COMMUNICATION BETWEEN THE MICROCONTROLLER AND AUDIO DEVICES LIKE MICROPHONES AND AMPLIFIERS.
- **INPUT SIDE:** A MICRO SD CARD WITH A 16-BIT, 44.1 KHz .WAV FILE HOLDS THE AUDIO.
- **OUTPUT SIDE:** INSTEAD OF USING THE ESP32'S 8-BIT DAC, A MAX98357A I2S AMPLIFIER PROVIDES HIGH-QUALITY OUTPUT.
- **I2S BASICS:**
 - **I2S PINS:** WORD SELECT, SERIAL CLOCK, AND SERIAL DATA.
 - THE ESP32 HAS CUSTOMIZABLE I2S PINS, AND WE CAN USE 44.1 KHz AND 16-BIT RESOLUTION.
 - THE WORD SELECT ALTERNATES BETWEEN LEFT AND RIGHT CHANNELS.
- **TESTING:** A MICROPHONE USING I2S IS CONNECTED, AND AUDIO SIGNALS ARE VISUALIZED ON AN OSCILLOSCOPE, CONFIRMING PROPER DATA TRANSMISSION.
- **CODE:** THE ESP32 CODE USES I2S TO READ MICROPHONE DATA AND SEND AUDIO DATA VIA SPI TO THE SD CARD AND I2S AMPLIFIER.
- **CONCLUSION:** I2S IS A SIMPLE, POWERFUL INTERFACE FOR HANDLING DIGITAL AUDIO, MAKING IT EASY TO INTEGRATE INTO PROJECTS FOR HIGH-QUALITY SOUND PLAYBACK.

18. IMPROVING ELECTRIC LONGBOARD PERFORMANCE WITH CAN BUS

- **PROBLEM:** WHEN TESTING THE ELECTRIC LONGBOARD, THE TWO HUB MOTORS DIDN'T SPIN SIMULTANEOUSLY AT THE SAME RPM DESPITE RECEIVING IDENTICAL PPM SIGNALS FROM THE REMOTE, LEADING TO MINOR MISALIGNMENT BETWEEN THE WHEELS.
- **SOLUTION:** THE CAN BUS IS USED TO SYNC THE TWO ELECTRONIC SPEED CONTROLLERS (ESCs) FOR PERFECT ALIGNMENT. THE VIDEO EXPLAINS HOW CAN BUS WORKS AND HOW IT WAS IMPLEMENTED FOR THIS FIX.

WHAT IS CAN BUS?

- **DEFINITION:** CAN (CONTROLLER AREA NETWORK) IS A TWO-WIRE COMMUNICATION SYSTEM USED FOR CONNECTING MULTIPLE DEVICES (NODES) WITHOUT NEEDING A HOST COMPUTER. IT'S MOSTLY USED IN AUTOMOTIVE SYSTEMS TO ALLOW DEVICES LIKE SENSORS, BUTTONS, AND MOTORS TO COMMUNICATE.
- **STRUCTURE:** THE CAN BUS USES TWO WIRES, CAN H (HIGH) AND CAN L (LOW), TO TRANSMIT DATA. IT USES A DIFFERENTIAL VOLTAGE BETWEEN THE TWO WIRES TO SEND MESSAGES EFFICIENTLY AND ROBUSTLY.

HOW CAN BUS WAS USED FOR ESCs:

1. **CONNECTING THE CAN BUS:** AFTER SOLDERING WIRES TO THE CAN PORTS OF THE ESCs, CAN FUNCTIONALITY WAS ACTIVATED IN THE ESC SOFTWARE.
2. **MESSAGE MODE:** THE CAN BUS WAS CONFIGURED IN THE SOFTWARE TO ENSURE BOTH ESCs SYNCHRONIZE THEIR MOTORS PERFECTLY.
3. **TEST:** AFTER DISCONNECTING THE RC INPUT FROM ONE ESC, BOTH MOTORS SPUN AT THE SAME RPM WITHOUT NOTICEABLE DIFFERENCES.

CAN BUS FRAME PROTOCOL:

- **VOLTAGE:** CAN H SWINGS UP TO A HIGH VOLTAGE, AND CAN L SWINGS DOWN TO LOW VOLTAGE. THE DIFFERENCE SHOULD BE ABOVE 2V FOR PROPER COMMUNICATION.
- **DOMINANCE AND RECESSIVE:** THE CAN SYSTEM USES A PRIORITY SYSTEM WHERE DOMINANT BITS (0) OVERRIDE RECESSIVE BITS (1). THIS ENSURES THAT DEVICES WITH LOWER IDs (HIGHER PRIORITY) CAN INTERRUPT AND CONTROL THE COMMUNICATION.

- **ERROR CHECKING: CAN USES A CYCLIC REDUNDANCY CHECK (CRC) AND ACKNOWLEDGMENT BITS TO VERIFY THE ACCURACY OF DATA TRANSMISSIONS.**

ADVANTAGES OF CAN BUS:

- **EFFICIENCY: ONLY TWO WIRES ARE NEEDED, REDUCING COST AND COMPLEXITY.**
- **ROBUSTNESS: THE DIFFERENTIAL VOLTAGE AND TWISTED PAIR WIRES ENSURE RELIABLE COMMUNICATION EVEN IN NOISY ENVIRONMENTS.**
- **PRIORITY SYSTEM: CAN USES AN ID-BASED PRIORITY SYSTEM TO PREVENT MESSAGE COLLISIONS, ENSURING THAT IMPORTANT DATA IS TRANSMITTED WITHOUT ERRORS.**
- **ERROR DETECTION: BUILT-IN ERROR-CHECKING MECHANISMS MAKE THE SYSTEM HIGHLY RELIABLE.**

KEY TAKEAWAYS:

- **THE CAN BUS ALLOWS DEVICES TO COMMUNICATE EFFICIENTLY, PREVENTING ERRORS AND ENSURING SYNCHRONIZED OPERATION, LIKE IN THE CASE OF THE ELECTRIC LONGBOARD ESCs.**
- **BY USING CAN FOR THE ESCs, THE BOARD ACHIEVES BETTER TRACTION, ESPECIALLY ON CHALLENGING TERRAINS LIKE CURVES OR MUDDY PATHS, THANKS TO SYNCHRONIZED WHEEL PERFORMANCE.**
- **CAN IS WIDELY USED IN AUTOMOTIVE SYSTEMS BUT CAN ALSO BE APPLIED IN VARIOUS OTHER PROJECTS, ESPECIALLY WHEN MULTIPLE DEVICES NEED TO COMMUNICATE RELIABLY AND EFFICIENTLY.**

19. MECHANICAL SEVEN-SEGMENT DISPLAYS WITH RS485 COMMUNICATION

THESE MECHANICAL SEVEN-SEGMENT DISPLAYS USE MOVING PLASTIC SEGMENTS CONTROLLED BY ELECTROMAGNETS THAT RETAIN THEIR POLARITY AFTER POWER IS CUT. THE CONTROL CIRCUIT USES AN ATMEGA32A MICROCONTROLLER, HIGH-VOLTAGE DRIVERS, AND DARLINGTON TRANSISTORS TO MANAGE THE ELECTROMAGNETS, MULTIPLEXING THEM TO DISPLAY NUMBERS.

THE DISPLAYS COMMUNICATE VIA RS485, AN ASYNCHRONOUS SERIAL PROTOCOL THAT USES TWO WIRES TO SEND DATA. THIS SYSTEM IS NOISE-RESISTANT DUE TO DIFFERENTIAL SIGNALING, MAKING IT RELIABLE OVER LONG DISTANCES.

TO INTERFACE WITH AN ARDUINO, AN RS485-TO-UART CONVERTER (MAX485) IS USED. THE ARDUINO SENDS DATA THROUGH THIS CONVERTER, CONTROLLING THE DISPLAY. THE ESP8266 CAN ALSO BE USED TO CREATE A SUBSCRIBER COUNTER, RETRIEVING YOUTUBE DATA AND DISPLAYING IT ON THE MECHANICAL SEVEN-SEGMENT DISPLAY.

20. UNDERSTANDING TRANSFORMERS AND THEIR DESIGN

TRANSFORMERS ARE ESSENTIAL COMPONENTS IN ELECTRICAL DEVICES, CONVERTING HIGH MAINS AC VOLTAGE INTO SAFE, LOWER AC VOLTAGES FOR COMMON DEVICES. THE BASIC STRUCTURE INCLUDES A METAL CORE MADE OF LAMINATED ELECTRICAL STEEL SHEETS AND TWO COILS: THE PRIMARY (INPUT) AND SECONDARY (OUTPUT).

WHEN AC VOLTAGE IS APPLIED TO THE PRIMARY COIL, IT GENERATES A CHANGING MAGNETIC FIELD, WHICH INDUCES A VOLTAGE IN THE SECONDARY COIL VIA THE PROCESS OF ELECTROMAGNETIC INDUCTION. THE OUTPUT VOLTAGE IS DETERMINED BY THE NUMBER OF WINDINGS IN BOTH COILS.

KEY CONCEPTS IN TRANSFORMER OPERATION:

- **MAGNETIC FLUX:** A CHANGING MAGNETIC FLUX INDUCES VOLTAGE IN THE SECONDARY COIL.
- **SELF-REGULATION:** THE TRANSFORMER REGULATES INPUT CURRENT TO BALANCE THE INDUCED VOLTAGE, MAINTAINING EFFICIENT OPERATION.
- **IRON LOSSES:** ENERGY IS LOST DUE TO EDDY CURRENTS AND HYSTERESIS IN THE IRON CORE.
- **EFFICIENCY:** THE EFFICIENCY OF A TRANSFORMER IS AFFECTED BY THE LOAD. HIGHER CURRENT LEADS TO MORE LOSSES AND LOWER EFFICIENCY.

WHEN A LOAD IS CONNECTED TO THE SECONDARY COIL, IT DRAWS CURRENT, WHICH INDUCES ADDITIONAL FLUX IN BOTH THE SECONDARY AND PRIMARY COILS. IF THE CURRENT EXCEEDS THE TRANSFORMER'S LIMITS, VOLTAGE DROPS, EFFICIENCY DECREASES, AND OVERHEATING CAN OCCUR, POTENTIALLY DAMAGING THE TRANSFORMER.

DESIGN CONSIDERATIONS:

- **CORE SIZE:** LARGER CORES CAN HANDLE MORE POWER, REDUCING LOSSES.
- **FREQUENCY:** HIGHER FREQUENCIES (USED IN SWITCHING POWER SUPPLIES) REDUCE CORE SIZE BUT INCREASE LOSSES IN CERTAIN MATERIALS.

- **MATERIAL CHOICE:** ELECTRICAL STEEL SHEETS ARE COMMONLY USED DUE TO THEIR HIGH MAGNETIC FLUX DENSITY, WHILE FERROMAGNETIC MATERIALS LIKE FERRITES ARE USED IN HIGH-FREQUENCY TRANSFORMERS.

21. UNDERSTANDING AUDIO CROSSOVERS AND FILTERS

IN THIS VIDEO, WE EXPLORE THE ROLE OF AUDIO CROSSOVERS IN LOUDSPEAKERS, EXPLAINING HOW THEY WORK AND HOW TO CALCULATE THEM. LET'S BREAK DOWN THE KEY POINTS:

1. PURPOSE OF AUDIO CROSSOVERS:

- **AUDIO SIGNALS, WHICH CONTAIN A BROAD RANGE OF FREQUENCIES (20 Hz TO 20,000 Hz), ARE AMPLIFIED BEFORE BEING SPLIT INTO TWO FREQUENCY BANDS FOR THE SPEAKERS: LOW FREQUENCIES (FOR WOOFERS) AND HIGH FREQUENCIES (FOR TWEETERS).**
- **THE WOOFER IS DESIGNED FOR LOW FREQUENCIES, WHILE THE TWEETER HANDLES HIGH FREQUENCIES. THE AUDIO CROSSOVER ENSURES THAT EACH SPEAKER RECEIVES ONLY THE FREQUENCIES IT'S BEST SUITED FOR.**

2. KEY COMPONENTS OF CROSSOVERS:

- **INDUCTORS AND CAPACITORS ARE USED TO FILTER OUT UNWANTED FREQUENCIES.**
 - **INDUCTORS ACT AS LOW-PASS FILTERS (ALLOWING LOW FREQUENCIES TO PASS WHILE BLOCKING HIGH ONES).**
 - **CAPACITORS ACT AS HIGH-PASS FILTERS (ALLOWING HIGH FREQUENCIES TO PASS WHILE BLOCKING LOW ONES).**

3. EXPERIMENT WITH FILTERS:

- **A SIMPLE RESISTOR WILL DAMPEN THE SIGNAL ACROSS ALL FREQUENCIES, BUT IT DOESN'T HELP SEPARATE HIGH AND LOW FREQUENCIES.**
- **AN INDUCTOR INCREASES ITS RESISTANCE AS FREQUENCY INCREASES, ACTING AS A LOW-PASS FILTER.**
- **A CAPACITOR DECREASES ITS RESISTANCE AT HIGHER FREQUENCIES, MAKING IT ACT AS A HIGH-PASS FILTER.**

4. RC AND RL FILTERS:

- **AN RC FILTER CONSISTS OF A RESISTOR AND CAPACITOR. IT'S A COMMON WAY TO BUILD LOW-PASS OR HIGH-PASS FILTERS.**

- **CUTOFF FREQUENCY: WHERE THE OUTPUT VOLTAGE IS REDUCED BY 3 dB (AROUND 0.707 TIMES THE INPUT VOLTAGE). FOR EXAMPLE, USING A 10 mF CAPACITOR AND A 10 Ω RESISTOR RESULTS IN A CUTOFF FREQUENCY OF AROUND 1591 Hz.**
- **RL FILTERS USE A RESISTOR AND INDUCTOR TO ACHIEVE SIMILAR EFFECTS, BUT THEY ARE LESS COMMONLY USED BECAUSE INDUCTORS ARE BULKIER AND MORE EXPENSIVE.**

5. WHY NOT JUST USE SIMPLE FILTERS?

- **FIRST-ORDER FILTERS (RC OR RL) ONLY ATTENUATE THE UNWANTED FREQUENCIES BY 20 dB PER DECADE, MEANING THEY TAKE TIME TO FULLY FILTER OUT NOISE.**
- **FOR FASTER AND MORE EFFICIENT FILTERING, SECOND-ORDER FILTERS ARE USED. THESE FILTERS USE A COMBINATION OF INDUCTORS AND CAPACITORS (LC FILTERS), INCREASING ATTENUATION TO 40 dB PER DECADE.**

6. REVERSE ENGINEERING THE OLD CROSSOVER:

- **AFTER REVERSE-ENGINEERING THE ORIGINAL CROSSOVER, WE FOUND IT USED A COMBINATION OF RLC COMPONENTS TO CREATE MORE PRECISE FILTERING.**
 - **THE ORIGINAL CROSSOVER HAD A LOW-PASS FILTER WITH A CUTOFF FREQUENCY OF 700 Hz AND A HIGH-PASS FILTER TUNED FOR THE TWEETER.**
 - **THE NEW CROSSOVER DIDN'T MATCH THE ORIGINAL DESIGN, WHICH AFFECTED SOUND QUALITY BECAUSE EACH LOUDSPEAKER REQUIRES A SPECIFIC FREQUENCY RESPONSE.**

7. CONCLUSION:

- **REPLACING THE ORIGINAL CROSSOVER WITH A GENERIC ONE WAS A MISTAKE BECAUSE EACH SPEAKER REQUIRES A CUSTOM-DESIGNED CROSSOVER TO ENSURE OPTIMAL SOUND QUALITY.**
- **YOU CAN DESIGN YOUR OWN CROSSOVER USING SIMULATION SOFTWARE LIKE WitWix CAT 2, WHICH ALLOWS YOU TO FINE-TUNE THE FILTERS ACCORDING TO THE SPEAKER'S FREQUENCY RESPONSE.**

KEY TAKEAWAYS:

- **AUDIO CROSSOVERS ARE CRITICAL FOR DIVIDING AUDIO SIGNALS INTO APPROPRIATE FREQUENCY BANDS FOR EACH SPEAKER.**
- **USING INDUCTORS, CAPACITORS, AND RESISTORS, DIFFERENT TYPES OF FILTERS CAN BE CREATED (LOW-PASS, HIGH-PASS, BAND-PASS).**

- **THE DESIGN OF CROSSOVERS IS COMPLEX, AND IT'S CRUCIAL TO MATCH THE SPEAKER'S FREQUENCY RESPONSE TO THE CROSSOVER FOR OPTIMAL PERFORMANCE.**

FINAL THOUGHTS: FILTERS AREN'T ONLY USED IN AUDIO SYSTEMS; THEY ALSO SERVE IN OTHER APPLICATIONS LIKE MAINS FILTERS AND CONVERTING PWM SIGNALS INTO PROPER SINE WAVES.

22. THIS VIDEO EXPLAINS HOW RFID AND NFC TECHNOLOGIES ARE USED FOR CONTACTLESS PAYMENTS, FOCUSING ON HOW THEY WORK AND THEIR SAFETY ASPECTS. IT STARTS BY INTRODUCING THREE POPULAR RFID READER ICs (RDM6300, PN532, RC522), FOLLOWED BY AN EXPLANATION OF HOW RFID WORKS WITH WIRELESS ENERGY TRANSFER AND DATA EXCHANGE BETWEEN THE READER AND THE TAG. THE VIDEO THEN DIFFERENTIATES NFC FROM RFID, HIGHLIGHTING ITS USE IN CONTACTLESS PAYMENTS WITH MORE STANDARDIZED PROTOCOLS AND SHORTER COMMUNICATION RANGES. THE AUTHOR ALSO DEMONSTRATES USING ARDUINO TO READ AND WRITE DATA TO RFID TAGS, SHOWING THE IMPORTANCE OF SECURITY IN CONTACTLESS PAYMENTS, AS DATA CAN BE ENCRYPTED. TO INCREASE SECURITY, AN ANTI-SKIMMING CARD HOLDER CAN BLOCK UNWANTED RFID SIGNALS.

23. WORKING PRINCIPLE OF COMPONENTS AND CIRCUIT

1. LED MATRIX:

- **THE MATRIX CONSISTS OF 384 LEDs ARRANGED IN 32 COLUMNS (X-DIRECTION) AND 12 ROWS (Y-DIRECTION).**
- **THE ANODES OF THE LEDs ARE CONNECTED TO PINS IN PARALLEL, CONTROLLING DIFFERENT ROWS OF LEDs.**

2. CONSTANT CURRENT LED DRIVERS (STP16C596 IC):

- **THESE ICs ARE RESPONSIBLE FOR CONTROLLING THE CATHODES OF THE LEDs. THEY SINK CURRENT THROUGH THE LEDs AND ALLOW CONSTANT CURRENT BASED ON THE SET RESISTOR VALUE.**
- **EACH IC HAS 16 OUTPUTS, WHICH MEANS THEY CAN CONTROL 16 LEDs, BUT THE MATRIX HAS MORE LEDs. TO ADDRESS THIS, MULTIPLEXING IS USED, WHERE THE ICs CONTROL LEDs IN CYCLES, RAPIDLY SWITCHING BETWEEN DIFFERENT ROWS (ANODE CONNECTIONS). THIS PROCESS IS QUICK ENOUGH THAT THE HUMAN EYE PERCEIVES A STABLE IMAGE.**

3. SHIFT REGISTERS (SIPO - SERIAL IN PARALLEL OUT):

- **SHIFT REGISTERS ARE USED TO MANAGE THE DATA FLOW TO CONTROL THE LEDs. THE DATA IS INPUT SERIALY (ONE BIT AT A TIME) AND THEN SHIFTED OUT IN PARALLEL TO CONTROL MULTIPLE OUTPUT PINS (16 IN THIS CASE).**
- **THIS ALLOWS CONTROLLING MANY LEDs USING ONLY TWO PINS FROM THE MICROCONTROLLER, SAVING GPIO PINS FOR OTHER TASKS.**

4. SCHMITT TRIGGER INVERTERS (74LS14):

- **THESE COMPONENTS ARE USED TO CLEAN UP THE DATA SIGNALS. THE SCHMITT TRIGGER ENSURES THAT ANY NOISY SIGNALS ARE PROPERLY INTERPRETED, MAKING THE SYSTEM MORE RELIABLE.**

WORKING OF THE CIRCUIT

- **MULTIPLEXING:**
 - **THIS TECHNIQUE IS USED TO CONTROL MORE LEDs THAN AVAILABLE PINS. BY RAPIDLY SWITCHING THE SUPPLY VOLTAGE ACROSS DIFFERENT ROWS AND USING SHIFT REGISTERS, THE SYSTEM CAN LIGHT UP INDIVIDUAL LEDs IN THE MATRIX. THE MULTIPLEXING SPEED IS FAST ENOUGH THAT THE HUMAN EYE PERCEIVES A STATIC IMAGE.**
- **CONTROL THROUGH MICROCONTROLLER (ARDUINO):**
 - **THE ARDUINO NANO IS USED TO CONTROL THE DATA SENT TO THE SHIFT REGISTERS, UTILIZING INTERRUPTS AND TIMERS TO MANAGE THE TIMING OF THE SIGNALS, CREATING A WORKING PATTERN ON THE MATRIX.**
 - **THE CODE CONTROLS THE SERIAL DATA INPUT, CLOCK PIN, AND LATCH PIN TO MANAGE THE SHIFT REGISTERS AND THUS CONTROL WHICH LEDs LIGHT UP.**

25. "UNDERSTANDING REACTIVE POWER, POWER FACTOR, AND ENERGY EFFICIENCY IN AC CIRCUITS"

KEY CONCEPTS:

- 1. REACTIVE POWER: POWER THAT OSCILLATES BETWEEN THE POWER SOURCE AND INDUCTIVE COMPONENTS (LIKE MOTORS AND TRANSFORMERS) BUT DOES NO USEFUL WORK. IT IS MEASURED IN VOLT-AMPERE REACTIVE (VAR).**

2. **POWER FACTOR:** A MEASURE OF HOW EFFECTIVELY THE POWER IS BEING USED. IT IS THE RATIO OF TRUE POWER (WATTS) TO APPARENT POWER (VOLT-AMPERES). A LOW POWER FACTOR MEANS MORE REACTIVE POWER IS BEING DRAWN, WHICH CAN STRESS POWER SYSTEMS.
3. **APPARENT POWER:** THE TOTAL POWER IN AN AC CIRCUIT, INCLUDING BOTH TRUE POWER (USEFUL) AND REACTIVE POWER (NON-USEFUL), MEASURED IN VOLT-AMPERES (VA).
4. **TRUE POWER:** THE ACTUAL USABLE POWER, WHICH IS MEASURED IN WATTS (W). THIS POWER DOES USEFUL WORK LIKE HEATING A RESISTOR OR TURNING A MOTOR.
5. **INDUCTIVE AND CAPACITIVE LOADS:** INDUCTIVE LOADS (E.G., MOTORS, TRANSFORMERS) CAUSE CURRENT TO LAG THE VOLTAGE, CREATING REACTIVE POWER. CAPACITIVE LOADS CAUSE CURRENT TO LEAD THE VOLTAGE AND CAN BE USED TO CANCEL OUT INDUCTIVE REACTIVE POWER.

CIRCUIT AND COMPONENT ROLES:

- **INDUCTIVE LOAD (E.G., TRANSFORMER/MOTOR):** DRAWS REACTIVE POWER, WHICH DOES NOT PERFORM USEFUL WORK BUT STILL REQUIRES CURRENT, LEADING TO INEFFICIENCY.
- **CAPACITOR:** USED TO CANCEL OUT INDUCTIVE REACTIVE POWER BY CREATING A PHASE SHIFT THAT OPPOSES THE INDUCTIVE CURRENT. THIS REDUCES OVERALL REACTIVE POWER IN THE SYSTEM.
- **ENERGY METER:** MEASURES BOTH THE TRUE AND APPARENT POWER OF AC APPLIANCES, AND CALCULATES THE POWER FACTOR. A LOW POWER FACTOR INDICATES HIGH REACTIVE POWER, WHICH IS UNDESIRABLE FOR GRID EFFICIENCY.

KEY TAKEAWAYS:

1. **POWER FACTOR:** A LOW POWER FACTOR MEANS MORE REACTIVE POWER, WHICH STRESSES THE POWER GRID, REQUIRING THICKER WIRES AND LARGER COMPONENTS TO HANDLE THE EXCESS CURRENT.
2. **REACTIVE POWER COMPENSATION:** CAPACITORS CAN HELP REDUCE THE REACTIVE POWER IN CIRCUITS, PARTICULARLY IN MOTORS. LARGER SYSTEMS USE AUTOMATIC POWER FACTOR CORRECTION (PFC) TO OPTIMIZE ENERGY USE.
3. **HARMONICS AND DEFORMED POWER:** MODERN POWER SUPPLIES, SUCH AS THOSE IN LAPTOPS, CAN DISTORT THE CURRENT WAVEFORM, ADDING HIGHER FREQUENCY HARMONICS. THIS CAN CREATE SIMILAR ISSUES AS REACTIVE POWER, LEADING TO INEFFICIENCY IN THE POWER GRID.

26. UNDERSTANDING SPI COMMUNICATION WITH ARDUINO AND DS3234 RTC IC

IN THIS VIDEO, THE FOCUS IS ON USING THE **SPI (SERIAL PERIPHERAL INTERFACE)** PROTOCOL WITH AN **ARDUINO** TO COMMUNICATE WITH THE **DS3234 REAL-TIME CLOCK (RTC) IC**. **UNLIKE I2C**, WHICH IS COMMONLY USED FOR COMMUNICATION WITH MULTIPLE SLAVE DEVICES, **SPI** WORKS DIFFERENTLY AND CAN ACHIEVE FASTER TRANSMISSION SPEEDS. THE **DS3234**, WHICH FEATURES **CLK, MISO, MOSI, AND SS** PINS INSTEAD OF THE TYPICAL **I2C PINS (SCL AND SDA)**, USES **SPI** FOR COMMUNICATION. HERE'S A BREAKDOWN OF THE VIDEO CONTENT:

1. SPI PROTOCOL BASICS:

- THE **SPI** PROTOCOL INVOLVES A MASTER DEVICE (**ARDUINO**) COMMUNICATING WITH A SLAVE DEVICE (**DS3234**) USING SPECIFIC PINS: **CLK (CLOCK)**, **MISO (MASTER IN SLAVE OUT)**, **MOSI (MASTER OUT SLAVE IN)**, AND **SS (SLAVE SELECT)**.
- THE CHIP SELECT (**CS**) PIN IS CRUCIAL, AS IT ENABLES COMMUNICATION WHEN PULLED LOW.

2. SPI INITIALIZATION:

- THE **SPI** LIBRARY IS USED IN **ARDUINO** CODE TO HANDLE THE COMMUNICATION.
- THE **CS** PIN IS SET AS AN OUTPUT PIN AND THE **SPI** PROTOCOL IS INITIALIZED.
- THE DATA TRANSMISSION IS SET TO "**MSB FIRST**" (**MOST SIGNIFICANT BIT FIRST**), AS PER THE **DS3234** DATASHEET.

3. SPI MODES:

- **SPI** OPERATES IN DIFFERENT MODES, PRIMARILY **MODE 0** AND **MODE 1** FOR MOST DEVICES. THE **DS3234** OPERATES IN **SPI MODE 1**, WHERE DATA IS READ ON THE FALLING EDGE OF THE CLOCK SIGNAL.
- THE CLOCK SIGNAL (**CLK**) IS GENERATED BY THE MASTER DEVICE (**ARDUINO**) TO SYNCHRONIZE DATA TRANSFER.

4. WRITING AND READING DATA:

- **WRITING DATA TO THE DS3234** INVOLVES SENDING AN ADDRESS AND DATA IN **HEXADECIMAL** FORMAT.
- A **BIT ADDRESS MAP** FOR THE **DS3234** IS REFERENCED, AND SPECIFIC BITS ARE SET TO CONTROL THE FEATURES OF THE **RTC**, SUCH AS **ENABLING SQUARE WAVE OUTPUTS**.

- **READING DATA FROM THE DS3234 REQUIRES SENDING THE ADDRESS FIRST, FOLLOWED BY READING THE DATA FROM THE SLAVE AND CONVERTING IT INTO A READABLE FORMAT.**

5. PRACTICAL EXAMPLE:

- **A SQUARE WAVE OUTPUT OF 8.192 KHz IS SUCCESSFULLY GENERATED BY THE DS3234, CONFIRMING THAT SPI COMMUNICATION IS WORKING CORRECTLY.**
- **THE TIME AND DATE ARE SET ON THE DS3234 BY CONVERTING THE INPUT VALUES INTO BINARY FORMAT AND WRITING THEM TO THE APPROPRIATE REGISTERS.**

6. FINAL THOUGHTS:

- **WHILE SPI COMMUNICATION CAN BE LIMITED BY THE NUMBER OF CHIP SELECT PINS AVAILABLE (UNLIKE I2C, WHICH CAN SUPPORT MULTIPLE DEVICES), IT OFFERS HIGHER TRANSMISSION SPEEDS, MAKING IT IDEAL FOR TASKS REQUIRING FAST DATA TRANSFER, SUCH AS WORKING WITH SD CARDS.**

BY THE END OF THE VIDEO, VIEWERS WILL UNDERSTAND HOW TO USE SPI WITH AN ARDUINO TO INTERACT WITH THE DS3234 RTC IC AND BE FAMILIAR WITH THE KEY DIFFERENCES BETWEEN SPI AND I2C PROTOCOLS.

27. UNDERSTANDING SCHMITT TRIGGERS AND THEIR APPLICATIONS

IN THIS VIDEO, THE FOCUS IS ON EXPLAINING THE CONCEPT OF SCHMITT TRIGGERS, WHICH ARE DESIGNED TO ADDRESS ISSUES LIKE NOISE AND BOUNCING IN SIGNAL TRANSITIONS THAT CAN OCCUR IN CIRCUITS USING OPERATIONAL AMPLIFIERS (OP-AMPS) OR DIGITAL INPUTS. HERE'S AN OVERVIEW OF THE KEY POINTS COVERED:

1. COMPARATOR VS. SCHMITT TRIGGER:

- **WHEN USING AN OP-AMP AS A COMPARATOR, A REFERENCE VOLTAGE (E.G., 2.5V) IS APPLIED TO THE INVERTING INPUT, AND A TRIANGULAR VOLTAGE BETWEEN 0 AND 5V IS APPLIED TO THE NON-INVERTING INPUT. THIS SETUP CAUSES THE OP-AMP TO OUTPUT A SQUARE WAVE.**
- **THE ISSUE WITH THIS SETUP IS THAT THE TRANSITION BETWEEN HIGH AND LOW STATES IS NOT CLEAN DUE TO NOISE OR OSCILLATIONS AROUND THE THRESHOLD VOLTAGE. SCHMITT TRIGGERS SOLVE THIS PROBLEM BY PROVIDING TWO THRESHOLD VOLTAGES (HIGH AND LOW) INSTEAD OF JUST ONE.**

2. FUNCTION OF A SCHMITT TRIGGER:

- **A SCHMITT TRIGGER INTRODUCES HYSTERESIS IN THE SIGNAL BY SETTING TWO DISTINCT THRESHOLDS. THE OUTPUT ONLY CHANGES IF THE INPUT VOLTAGE SURPASSES THE HIGH THRESHOLD OR DROPS BELOW THE LOW THRESHOLD.**
- **THIS HYSTERESIS PREVENTS UNNECESSARY SWITCHING DUE TO NOISE OR MINOR FLUCTUATIONS WITHIN THE THRESHOLD RANGE, LEADING TO MORE STABLE SIGNAL TRANSITIONS.**

3. NON-INVERTING AND INVERTING SCHMITT TRIGGERS:

- **A NON-INVERTING SCHMITT TRIGGER WILL PULL THE OUTPUT HIGH WHEN THE INPUT SURPASSES THE HIGH THRESHOLD AND PULL IT LOW WHEN THE INPUT DROPS BELOW THE LOW THRESHOLD.**
- **AN INVERTING SCHMITT TRIGGER WORKS SIMILARLY BUT INVERTS THE OUTPUT STATES FOR THE HIGH AND LOW THRESHOLDS.**

4. PRACTICAL EXAMPLE WITH 74 HC 14 HEX INVERTING SCHMITT TRIGGER IC:

- **THE 74 HC 14 IS A POPULAR SCHMITT TRIGGER IC THAT CAN BE EASILY USED IN CIRCUITS. IT HAS SIX DATA INPUT PINS AND CORRESPONDING OUTPUT PINS. THE DATASHEET PROVIDES THE THRESHOLD VOLTAGES, WHICH FOR THE IC WERE MEASURED AROUND 2.1V AND 3.1V.**
- **USING THE IC IN CIRCUITS ALLOWS FOR SHARP AND CLEAN TRANSITIONS EVEN WHEN THE INPUT SIGNAL IS NOISY OR UNSTABLE.**

5. APPLICATIONS OF SCHMITT TRIGGERS:

- **PUSH-BUTTON DEBOUNCING: WHEN USING A MECHANICAL PUSH-BUTTON AS AN INPUT, YOU MAY ENCOUNTER BOUNCING DURING THE TRANSITION FROM LOW TO HIGH STATES. THIS CAN LEAD TO ERRATIC BEHAVIOR. BY ADDING AN RC NETWORK TO SMOOTH THE SIGNAL AND FOLLOWING IT UP WITH A SCHMITT TRIGGER, YOU CAN ACHIEVE A CLEAN SIGNAL TRANSITION.**
- **MICROCONTROLLER INPUTS: MICROCONTROLLERS ALREADY HAVE BUILT-IN SCHMITT TRIGGER LOGIC FOR DIGITAL INPUTS. THIS HELPS IN HANDLING NOISY SIGNALS WITHOUT THE NEED FOR ADDITIONAL SCHMITT TRIGGER COMPONENTS.**
- **RELAXATION OSCILLATOR: SCHMITT TRIGGERS CAN BE USED WITH CAPACITORS AND RESISTORS TO CREATE A SIMPLE RELAXATION OSCILLATOR THAT CONTINUOUSLY CHARGES AND DISCHARGES THE CAPACITOR, GENERATING A SQUARE WAVE OUTPUT. BY ADJUSTING THE RESISTANCE WITH A POTENTIOMETER, YOU CAN TUNE THE FREQUENCY TO THE KILOHERTZ RANGE.**

- **SIGNAL CONDITIONING: SCHMITT TRIGGERS ARE USEFUL FOR CLEANING UP NOISY OR WORN-OUT DATA SIGNALS, ENSURING THEY HAVE SHARP TRANSITIONS AND ARE EASIER TO PROCESS.**

6. CONCLUSION:

- **SCHMITT TRIGGERS ARE ESSENTIAL COMPONENTS WHEN WORKING WITH NOISY SIGNALS OR WHEN YOU NEED CLEAN, SHARP TRANSITIONS IN DIGITAL CIRCUITS. THEY ARE COMMONLY USED IN APPLICATIONS LIKE PUSH-BUTTON DEBOUNCING, OSCILLATORS, AND SIGNAL CONDITIONING.**

29. UNDERSTANDING STRAIN GAUGES AND LOAD CELLS FOR WEIGHT MEASUREMENT

IN THIS VIDEO, WE TAKE A DEEPER DIVE INTO THE WORLD OF STRAIN GAUGES AND LOAD CELLS, EXPLORING HOW THEY CAN BE USED TO MEASURE WEIGHT AND FORCE. SPECIFICALLY, WE'LL FOCUS ON THE INTEGRATION OF THESE COMPONENTS IN A REAL-WORLD APPLICATION—AN ELECTRIC LONGBOARD WITH A WEIGHT MEASURING SYSTEM THAT AUTOMATICALLY DETECTS WHEN THE RIDER HAS LOST CONTROL. LET'S BREAK DOWN THE KEY CONCEPTS DISCUSSED:

1. WHAT IS A STRAIN GAUGE?

- **A STRAIN GAUGE IS A RESISTIVE ELEMENT TYPICALLY ATTACHED TO A SURFACE TO MEASURE THE STRAIN (OR DEFORMATION) OF THAT SURFACE. WHEN THE SURFACE EXPERIENCES A FORCE, THE STRAIN GAUGE DEFORMS, CAUSING A SMALL CHANGE IN ITS RESISTANCE. THIS CHANGE IS PROPORTIONAL TO THE FORCE OR WEIGHT APPLIED.**

2. STRAIN GAUGE CONSTRUCTION:

- **STRAIN GAUGES TYPICALLY CONSIST OF A ZIG-ZAG PATTERN OF RESISTANCE WIRE THAT IS SECURED TO A FLEXIBLE PIECE OF PLASTIC. THE STANDARD RESISTANCE VALUE FOR THESE GAUGES IS OFTEN 120 OHMS, BUT OTHER VALUES LIKE 350, 700, OR 1000 OHMS CAN ALSO BE FOUND DEPENDING ON THE APPLICATION.**

3. MEASURING WEIGHT WITH STRAIN GAUGES:

- **STRAIN GAUGES ARE GLUED TO THE OBJECT WHOSE WEIGHT OR FORCE YOU WANT TO MEASURE. WHEN FORCE IS APPLIED, THE STRAIN GAUGE'S RESISTANCE CHANGES SLIGHTLY. HOWEVER, THE CHANGE IN RESISTANCE IS TYPICALLY VERY SMALL AND**

HARD TO MEASURE DIRECTLY, WHICH IS WHERE THE **WHEATSTONE BRIDGE** COMES INTO PLAY.

4. THE WHEATSTONE BRIDGE:

- **THE WHEATSTONE BRIDGE CIRCUIT ALLOWS US TO CONVERT THE SMALL CHANGE IN RESISTANCE INTO A MEASURABLE VOLTAGE DIFFERENCE. IN THIS CONFIGURATION, THE STRAIN GAUGE IS ONE PART OF THE BRIDGE, AND THE OTHER RESISTORS ARE PRECISION RESISTORS (LIKE 120 OHMS). WHEN NO FORCE IS APPLIED, THE VOLTAGE DIFFERENCE IS ZERO. WHEN FORCE IS APPLIED, THE VOLTAGE DIFFERENCE BECOMES PROPORTIONAL TO THE STRAIN.**

5. AMPLIFICATION AND SIGNAL PROCESSING:

- **THE VOLTAGE DIFFERENCE PRODUCED BY THE WHEATSTONE BRIDGE IS TYPICALLY VERY SMALL, SO IT NEEDS TO BE AMPLIFIED. A DIFFERENTIAL OP-AMP CIRCUIT CAN BE USED TO AMPLIFY THE SIGNAL, MAKING IT READABLE BY THE ANALOG-TO-DIGITAL CONVERTER (ADC) OF A MICROCONTROLLER.**
- **A COMMON ISSUE WITH STRAIN GAUGES IS THEIR SENSITIVITY TO TEMPERATURE CHANGES, WHICH CAN AFFECT THE RESISTANCE AND THUS THE VOLTAGE DIFFERENCE. TO COMPENSATE FOR THIS, A HALF-BRIDGE CONFIGURATION IS OFTEN USED, WHERE TWO STRAIN GAUGES ARE EMPLOYED TO BALANCE OUT TEMPERATURE-RELATED ERRORS.**

6. LOAD CELLS: A SIMPLIFIED SOLUTION:

- **INSTEAD OF BUILDING A STRAIN GAUGE CIRCUIT FROM SCRATCH, A LOAD CELL CAN BE USED. A LOAD CELL IS ESSENTIALLY AN ALUMINUM PROFILE WITH A BUILT-IN WHEATSTONE BRIDGE AND STRAIN GAUGES. IT SIMPLIFIES THE SETUP AS YOU ONLY NEED TO CONNECT THE LOAD CELL TO A POWER SOURCE AND MEASURE THE OUTPUT VOLTAGE.**
- **TO MEASURE THIS VOLTAGE, A SIMPLE AMPLIFIER CIRCUIT CAN BE USED, OR YOU CAN USE SPECIALIZED ICs LIKE THE HX711, A 24-BIT ADC WITH AN INTEGRATED AMPLIFIER.**

7. USING THE HX711 WITH ARDUINO:

- **THE HX711 IC IS PARTICULARLY USEFUL WHEN WORKING WITH LOAD CELLS. IT CAN AMPLIFY THE SIGNAL FROM THE LOAD CELL AND OUTPUT A HIGHLY PRECISE READING THROUGH ITS 24-BIT ADC. THIS ALLOWS FOR EXTREMELY FINE MEASUREMENTS, DETECTING EVEN THE SMALLEST CHANGES IN WEIGHT.**

- **BY CONNECTING THE HX711 TO AN ARDUINO, WE CAN EASILY READ THE MEASUREMENTS AND OUTPUT THEM TO THE SERIAL MONITOR FOR FURTHER PROCESSING. THE 24-BIT RESOLUTION PROVIDES A SIGNIFICANTLY HIGHER LEVEL OF DETAIL COMPARED TO THE STANDARD 10-BIT ADC FOUND IN MICROCONTROLLERS LIKE THE ATMEGA328P.**

8. PRACTICAL APPLICATION IN THE LONGBOARD:

- **IN THE CASE OF THE ELECTRIC LONGBOARD, THE STRAIN GAUGE OR LOAD CELL IS USED TO DETECT THE RIDER'S WEIGHT. IF THE RIDER LOSES CONTROL AND JUMPS OFF, THE SYSTEM AUTOMATICALLY DETECTS THE CHANGE IN WEIGHT AND ENGAGES THE BRAKES.**

9. CONCLUSION:

- **STRAIN GAUGES AND LOAD CELLS ARE CRUCIAL COMPONENTS FOR FORCE AND WEIGHT MEASUREMENT IN VARIOUS APPLICATIONS. WHETHER YOU'RE BUILDING A CUSTOM WEIGHT SENSING SYSTEM OR USING READY-MADE LOAD CELLS, THESE SENSORS OFFER A SIMPLE YET EFFECTIVE WAY TO MEASURE FORCE IN A WIDE RANGE OF PROJECTS.**

30. RELAYS VS OPTOCOUPERS: KEY DIFFERENCES AND USES

RELAYS AND OPTOCOUPERS ARE ESSENTIAL FOR CONTROLLING HIGH-VOLTAGE APPLIANCES WITH LOW-VOLTAGE SIGNALS. HERE'S A QUICK BREAKDOWN:

RELAYS:

- **FUNCTION: ELECTROMECHANICAL SWITCHES THAT USE A COIL TO CREATE A MAGNETIC FIELD, CLOSING CONTACTS TO CONTROL HIGH-VOLTAGE CIRCUITS.**
- **ADVANTAGES: PROVIDE GALVANIC ISOLATION BETWEEN CONTROL AND LOAD CIRCUITS, MAKING THEM SAFE FOR CONTROLLING HIGH-VOLTAGE DEVICES.**
- **LIMITATIONS: SLOW, WITH CONTACTS THAT WEAR OUT OVER TIME.**

OPTOCOUPERS:

- **FUNCTION: USE AN LED AND A PHOTSENSITIVE SENSOR (USUALLY A TRANSISTOR OR TRIAC) TO TRANSMIT SIGNALS ACROSS AN ISOLATED GAP.**

- **ADVANTAGES: FASTER THAN RELAYS, REQUIRE LESS CURRENT TO ACTIVATE, AND ALSO PROVIDE GALVANIC ISOLATION.**
- **LIMITATIONS: CAN'T HANDLE LARGE LOADS LIKE RELAYS.**

IN CONCLUSION, RELAYS ARE GREAT FOR SWITCHING LARGE LOADS, WHILE OPTOCOUPERS ARE FASTER AND USED FOR MORE PRECISE CONTROL, OFTEN ALONGSIDE RELAYS IN COMPLEX SYSTEMS.

31.SCHOTTKY VS ZENER DIODES: DIFFERENCES AND USES

DIODES ARE FUNDAMENTAL COMPONENTS IN ELECTRONICS, BUT SCHOTTKY AND ZENER DIODES HAVE UNIQUE CHARACTERISTICS. HERE'S A QUICK BREAKDOWN OF BOTH:

SCHOTTKY DIODES:

- **LOW FORWARD VOLTAGE DROP: SCHOTTKY DIODES HAVE A SMALLER VOLTAGE DROP (~0.45V), LEADING TO LESS POWER LOSS COMPARED TO REGULAR DIODES (~0.87V).**
- **FAST SWITCHING: IDEAL FOR HIGH-FREQUENCY APPLICATIONS LIKE BOOST CONVERTERS, AS THEY CAN OPERATE AT UP TO 100 KHz AND BEYOND.**
- **LIMITATIONS: LOWER BLOCKING VOLTAGE AND HIGHER REVERSE LEAKAGE CURRENT THAN STANDARD DIODES.**
- **USE CASE: GREAT FOR REVERSE VOLTAGE PROTECTION, HIGH-FREQUENCY CIRCUITS, AND EFFICIENT RECTIFICATION.**

ZENER DIODES:

- **REVERSE BIAS OPERATION: ZENER DIODES ARE TYPICALLY USED IN REVERSE BIAS, WHERE THEY MAINTAIN A CONSTANT VOLTAGE ONCE THE APPLIED VOLTAGE EXCEEDS THE ZENER VOLTAGE.**
- **VOLTAGE REGULATION: OFTEN USED FOR VOLTAGE REGULATION OR REFERENCE, SUCH AS PROVIDING A 5.1V REGULATOR OR PROTECTING SENSITIVE COMPONENTS LIKE MOSFETS FROM OVERVOLTAGE.**
- **LIMITATIONS: NOT PRECISE UNDER VARYING INPUT VOLTAGE OR TEMPERATURE, AND CURRENT DRAW MUST BE CONTROLLED TO AVOID VOLTAGE COLLAPSE.**
- **USE CASE: VOLTAGE CLIPPING OR REGULATION, AND PROTECTION CIRCUITS.**

CONCLUSION:

- **SCHOTTKY DIODES:** LOW VOLTAGE DROP AND FAST SWITCHING, IDEAL FOR HIGH-FREQUENCY APPLICATIONS.
- **ZENER DIODES:** VOLTAGE REGULATION AND PROTECTION, PARTICULARLY IN REVERSE BIAS.

BOTH DIODES ARE INDISPENSABLE IN THEIR OWN RIGHT FOR SPECIFIC TASKS.

32. UNDERSTANDING TIMERS IN MICROCONTROLLERS FOR PRECISE TIMING EVENTS

WHEN WORKING WITH MICROCONTROLLERS, PRECISE TIMING EVENTS ARE CRUCIAL, LIKE IN AN ALARM CLOCK PROJECT WHERE TASKS LIKE COUNTING SECONDS, UPDATING A DISPLAY, OR GENERATING A PWM SIGNAL ARE NECESSARY. MICROCONTROLLERS LIKE THE ATMEGA328P (USED IN ARDUINO) HAVE BUILT-IN TIMERS THAT ALLOW THESE EVENTS TO HAPPEN EFFICIENTLY WITHOUT BLOCKING THE MAIN PROGRAM.

BASIC TIMER CONCEPT:

MICROCONTROLLERS HAVE PERIPHERALS LIKE TIMERS THAT RUN INDEPENDENTLY, ALLOWING THE CPU TO CONTINUE EXECUTING OTHER TASKS WITHOUT DELAYS. FOR EXAMPLE, ARDUINO'S 16-BIT TIMER 1 CAN COUNT UP TO 65,535, TRIGGERING EVENTS ON OVERFLOW. YOU CAN CONFIGURE THE TIMER TO GENERATE INTERRUPTS FOR TIMED EVENTS WITHOUT DELAYING THE MAIN PROGRAM LOOP.

EXAMPLE - BLINKING AN LED:

USING A SIMPLE ARDUINO SKETCH, AN LED CAN BLINK EVERY SECOND USING THE DELAY() FUNCTION. HOWEVER, DELAY() BLOCKS THE PROGRAM, MAKING IT UNRESPONSIVE TO INPUTS. THIS ISSUE IS SOLVED BY USING TIMER 1, WHICH RUNS IN THE BACKGROUND TO TRIGGER EVENTS WHILE THE MAIN LOOP REMAINS FREE.

USING PRE-SCALING AND TIMER INTERRUPTS:

- **PRE-SCALING ADJUSTS THE TIMER'S CLOCK SPEED, ALLOWING LONGER INTERVALS BETWEEN INTERRUPTS.**
- **EXAMPLE: WITH A PRESCALER OF 256, TIMER 1 OVERFLOWS APPROXIMATELY EVERY 1.04 SECONDS.**
- **BY ADJUSTING THE STARTING VALUE OF THE TIMER, PRECISE TIMING CAN BE ACHIEVED.**

CTC MODE (CLEAR TIMER ON COMPARE MATCH):

IN CTC MODE, THE TIMER COMPARES ITS COUNTER VALUE WITH A PREDEFINED REGISTER VALUE (OCR1A/B) AND GENERATES INTERRUPTS WHEN THEY MATCH. THIS ENABLES PRECISE TIMING FOR MULTIPLE INTERVALS, SUCH AS 1/4 SECOND AND 1/2 SECOND, USING TWO INDEPENDENT COMPARE INTERRUPTS.

PWM GENERATION:

TIMERS CAN ALSO GENERATE PWM SIGNALS. BY SETTING SPECIFIC BITS, PWM CAN BE OUTPUT ON PINS (LIKE PIN 9 AND PIN 10) WITH ADJUSTABLE DUTY CYCLES. THIS IS USEFUL FOR CONTROLLING THINGS LIKE MOTOR SPEED OR DIMMING LEDs.

FAST PWM MODE:

IN FAST PWM MODE, THE COUNTER RUNS UP TO 255, AND THE OUTPUT PINS TOGGLE BASED ON THE TIMER'S COMPARISON VALUE. BY ADJUSTING THE PWM FREQUENCY (E.G., UP TO 62.5 kHz WITH A PRESCALER OF 1), YOU CAN CONTROL SIGNALS WITH A VARIABLE DUTY CYCLE. FOR EVEN HIGHER FREQUENCIES (UP TO 8 MHz), THE ICR1 REGISTER CAN BE USED AS THE TOP VALUE.

CONCLUSION:

MICROCONTROLLER TIMERS ARE POWERFUL TOOLS FOR CREATING PRECISE, NON-BLOCKING TIMING EVENTS. WHETHER IT'S GENERATING PWM SIGNALS, TIMING EVENTS FOR CLOCKS, OR CONTROLLING DISPLAYS, TIMERS LET YOU HANDLE MULTIPLE TASKS SIMULTANEOUSLY WHILE KEEPING YOUR CODE RESPONSIVE.

34. MOSFETs vs. IGBTs FOR SOLID-STATE TESLA COILS

WHEN DESIGNING CIRCUITS FOR A SOLID-STATE TESLA COIL (SSTC), CHOOSING BETWEEN MOSFETs AND IGBTs IS CRUCIAL. BOTH ARE USED AS SWITCHES, BUT THEY HAVE KEY DIFFERENCES.

BASIC DIFFERENCES:

- **MOSFETs ARE FAST, EFFICIENT SWITCHES IDEAL FOR LOW-TO-MEDIUM VOLTAGE APPLICATIONS.**
- **IGBTs COMBINE THE HIGH-SPEED SWITCHING OF MOSFETs WITH THE HIGH-CURRENT AND VOLTAGE CAPABILITIES OF BJTs, MAKING THEM SUITABLE FOR MEDIUM-TO-HIGH VOLTAGE APPLICATIONS.**

KEY FEATURES:

- **MOSFETs: FASTER SWITCHING SPEEDS (32 NS RISE TIME, 160 NS FALL TIME) AND LOWER POWER LOSS AT LOWER CURRENTS (0.04 W AT 1.7 A).**
- **IGBTs: SLOWER SWITCHING SPEEDS (145 NS RISE TIME, 240 NS FALL TIME) BUT HANDLE HIGHER CURRENTS EFFICIENTLY, WITH HIGHER VOLTAGE DROPS (1.3 W AT 1.65 A).**

WHICH TO USE:

- **MOSFETs ARE IDEAL FOR HIGH-FREQUENCY (ABOVE 200 KHz) AND LOW-TO-MEDIUM VOLTAGE APPLICATIONS DUE TO THEIR FAST SWITCHING AND LOW LOSSES.**
- **IGBTs ARE BETTER FOR LOW-FREQUENCY (BELOW 200 KHz) AND HIGH-CURRENT, HIGH-VOLTAGE APPLICATIONS, WHERE THEIR ABILITY TO MANAGE LARGE LOADS IS MORE BENEFICIAL.**

IN SUMMARY, USE MOSFETs FOR HIGHER FREQUENCIES AND LOWER CURRENTS, AND IGBTs FOR HIGH-VOLTAGE, HIGH-CURRENT SCENARIOS.

35. IN THIS VIDEO, WE EXPLORE THE ANALOG-TO-DIGITAL CONVERTER (ADC), WHICH IS RESPONSIBLE FOR CONVERTING AN ANALOG SIGNAL INTO A DIGITAL VALUE. LET'S BREAK DOWN THE KEY ASPECTS:

1. SAMPLING RATE:

- **THE SAMPLING RATE DETERMINES HOW FREQUENTLY THE ADC SAMPLES THE INPUT SIGNAL.**
- **NYQUIST-SHANNON THEOREM SUGGESTS THAT THE SAMPLING RATE SHOULD BE AT LEAST TWICE THE SIGNAL FREQUENCY TO ACCURATELY RECONSTRUCT THE WAVEFORM. A COMMON RULE IS TO USE A SAMPLING RATE 10 TIMES HIGHER THAN THE SIGNAL FREQUENCY FOR BETTER ACCURACY.**
- **FOR EXAMPLE, IF YOU WANT TO SAMPLE A 10 KHz SIGNAL, A SAMPLING RATE OF 100 KHz IS IDEAL.**

2. RESOLUTION:

- **RESOLUTION REFERS TO HOW FINELY THE ADC CAN DIFFERENTIATE BETWEEN VOLTAGES. IT'S REPRESENTED BY THE NUMBER OF BITS THE ADC USES.**
- **A 4-BIT ADC HAS 16 POSSIBLE VALUES (0 TO 15), SO IT GIVES LARGER STEPS BETWEEN SAMPLED VALUES, LEADING TO LESS ACCURACY.**

- **A 10-BIT ADC (LIKE ARDUINO'S) HAS 1024 POSSIBLE VALUES, RESULTING IN SMALLER STEPS AND BETTER ACCURACY.**
- **A 12-BIT ADC (LIKE THE ADS7816) HAS 4096 POSSIBLE VALUES, PROVIDING THE HIGHEST PRECISION.**

3. How ADC Works:

- **THE ARDUINO ADC USES A METHOD CALLED SUCCESSIVE APPROXIMATION (SAR). THE PROCESS INCLUDES:**
 - 1. SAMPLING THE INPUT VOLTAGE.**
 - 2. USING A COMPARATOR TO COMPARE IT AGAINST A REFERENCE VOLTAGE.**
 - 3. ITERATIVELY ADJUSTING THE BINARY VALUE UNTIL IT CLOSELY MATCHES THE INPUT VOLTAGE.**
- **THE RESOLUTION AFFECTS HOW FINE THE VOLTAGE STEPS ARE. FOR INSTANCE, WITH A 5V REFERENCE, A 4-BIT ADC HAS VOLTAGE STEPS OF 312.5 mV, WHILE A 10-BIT ADC HAS 4.88 mV STEPS, AND A 12-BIT ADC HAS 1.22 mV STEPS.**

4. DIY ADCs:

- **WHILE YOU CAN USE EXTERNAL ICs LIKE THE ADS7816 FOR HIGH PRECISION, A FLASH ADC CAN BE BUILT DIY. IT USES COMPARATORS AND A RESISTOR NETWORK TO QUICKLY CONVERT ANALOG SIGNALS TO DIGITAL VALUES, THOUGH WITH LIMITED RESOLUTION (E.G., 2-BIT OR 8-BIT).**

CONCLUSION:

- **THE KEY SPECIFICATIONS FOR CHOOSING AN ADC ARE SAMPLING RATE AND RESOLUTION.**
- **FOR DIY PROJECTS, YOU MIGHT CONSIDER BUILDING A FLASH ADC FOR SPEED, BUT FOR BETTER PRECISION, USING AN EXTERNAL ADC IC LIKE THE ADS7816 WITH AN ARDUINO IS A GREAT OPTION.**

36. OVERVIEW OF THE 555 TIMER IC

THE 555 TIMER IC IS ONE OF THE MOST POPULAR COMPONENTS IN ELECTRONICS, USED IN VARIOUS APPLICATIONS LIKE TIMING, PULSE GENERATION, AND SWITCHING.

KEY PINS:

- **PINS 1 & 8: VOLTAGE DIVIDER BETWEEN GROUND AND SUPPLY VOLTAGE.**

- **PIN 2 (TRIGGER):** STARTS THE TIMER WHEN VOLTAGE IS APPLIED.
- **PIN 3 (OUTPUT):** PROVIDES THE OUTPUT SIGNAL.
- **PIN 4 (RESET):** RESETS THE INTERNAL FLIP-FLOP WHEN GROUNDED.
- **PIN 5 (CONTROL VOLTAGE):** ADJUSTS OR STABILIZES REFERENCE VOLTAGES.
- **PIN 6 (THRESHOLD):** MONITORS THE CAPACITOR'S VOLTAGE.
- **PIN 7 (DISCHARGE):** DISCHARGES THE CAPACITOR WHEN TRIGGERED.

CONFIGURATIONS:

1. **MONOSTABLE (ONE-SHOT):** GENERATES A SINGLE HIGH PULSE WHEN TRIGGERED, FOLLOWED BY A LOW OUTPUT. IDEAL FOR DELAY CIRCUITS.
2. **BISTABLE (FLIP-FLOP):** PRODUCES TWO STABLE OUTPUT STATES (HIGH/LOW), GREAT FOR ON/OFF SWITCHING WITH A BUTTON.
3. **ASTABLE (OSCILLATOR):** CREATES A CONTINUOUS SQUARE WAVE, USEFUL FOR GENERATING PWM SIGNALS. THE CMOS 555 IMPROVES SYMMETRY AND EFFICIENCY OVER THE STANDARD 555.

ADJUSTING DUTY CYCLE:

YOU CAN ACHIEVE A 50% DUTY CYCLE FOR PWM BY USING DIODES AND A POTENTIOMETER TO CONTROL CHARGING AND DISCHARGING CURRENTS.

THE 555 TIMER IC IS AN ESSENTIAL, VERSATILE COMPONENT IN MANY ELECTRONIC PROJECTS.

37. SERVO MOTORS: OVERVIEW AND USAGE

SERVOS ARE WIDELY USED IN PROJECTS FOR PRECISE MOTOR CONTROL. THEY COMBINE A MOTOR WITH BUILT-IN ELECTRONICS, MAKING THEM EASY TO USE.

HOW SERVOS WORK:

- **WIRING: SERVOS HAVE THREE WIRES:**
 - **BROWN: GROUND**
 - **RED: VCC (4.8-7.2V)**
 - **ORANGE: PWM CONTROL SIGNAL**
- **CONTROL SIGNAL: A 50Hz PWM SIGNAL WITH A 1-2MS PULSE WIDTH CONTROLS THE MOTOR'S POSITION (1MS = -90°, 1.5MS = 0°, 2MS = +90°).**

- **INSIDE THE SERVO:**

- **GEARS REDUCE MOTOR SPEED AND INCREASE TORQUE.**
- **A POTENTIOMETER PROVIDES POSITION FEEDBACK TO THE CONTROL IC.**

SERVOs ARE SIMPLE TO USE WITH A MICROCONTROLLER, LIKE AN ARDUINO, OR WITH A 555 TIMER TO GENERATE THE PWM SIGNAL. FOR 360° ROTATION, MODIFY THE SERVO BY REMOVING THE MECHANICAL STOP AND FEEDBACK POTENTIOMETER.

38. HOW STEPPER MOTORS WORK

STEPPER MOTORS ARE USED FOR PRECISE CONTROL IN APPLICATIONS LIKE 3D PRINTING. THEY MOVE IN DISCRETE STEPS, OFFERING ACCURATE POSITIONING.

KEY COMPONENTS:

- **ROTOR & STATOR: THE ROTOR HAS PERMANENT MAGNETS, WHILE THE STATOR HAS COILS THAT GENERATE MAGNETIC FIELDS WHEN POWERED.**
- **COILS: TWO COIL PAIRS CREATE ALTERNATING MAGNETIC POLES TO MOVE THE ROTOR STEP-BY-STEP.**

How It Works:

- **COILS ARE POWERED ALTERNATELY, MOVING THE ROTOR BY A FIXED ANGLE (E.G., 1.8° PER STEP).**
- **COMMON DRIVING METHODS INCLUDE WAVE DRIVING, FULL-STEP, AND HALF-STEP, WITH MICROSTEPPING FOR SMOOTHER MOVEMENT.**

CONTROL:

- **THE A4988 DRIVER IC ALLOWS PRECISE MICROSTEPPING CONTROL.**
- **A 555 TIMER CAN GENERATE THE SIGNALS TO CONTROL THE MOTOR.**

ADVANTAGES:

- **STEPPER MOTORS PROVIDE PRECISE POSITIONING AND HOLD THEIR POSITION WITHOUT POWER, MAKING THEM IDEAL FOR TASKS LIKE 3D PRINTING. MICROSTEPPING ENSURES SMOOTHER AND QUIETER OPERATION.**

39. How MOSFETs Improve Efficiency Over BJTs

IN PREVIOUS VIDEOS, WE SAW HOW BIPOLAR JUNCTION TRANSISTORS (BJTs) WORK AS SWITCHES, BUT THEY TEND TO HEAT UP WHEN CONTROLLING LARGER LOADS, LOWERING EFFICIENCY. MOSFETs, HOWEVER, ARE MORE EFFICIENT, WITH MINIMAL ENERGY LOSS, MAKING THEM IDEAL FOR HIGHER POWER APPLICATIONS.

MOSFET BASICS:

- **TYPES:** THERE ARE TWO MAIN TYPES—N-CHANNEL AND P-CHANNEL. N-CHANNEL MOSFETs, LIKE THE IRLZ44N, ARE MORE COMMONLY USED.
- **OPERATION:** MOSFETs ARE VOLTAGE-CONTROLLED DEVICES. UNLIKE BJTs, THEY DON'T RELY ON CURRENT AT THE GATE BUT NEED A HIGH ENOUGH VOLTAGE TO TURN ON. FOR EXAMPLE, A 5V SIGNAL CAN CONTROL UP TO 5A OF CURRENT.

BUILDING A BASIC CIRCUIT:

- **N-CHANNEL MOSFET:** CONNECT THE SOURCE TO GROUND, THE CATHODE OF THE LOAD (LED OR LIGHT BULB) TO THE DRAIN, AND THE ANODE TO THE SUPPLY VOLTAGE. A 10k Ω PULL-DOWN RESISTOR AT THE GATE PREVENTS ACCIDENTAL ACTIVATION.
- **CONTROL:** USING THE PWM SIGNAL FROM AN ARDUINO, THE MOSFET ACTS AS A SWITCH, AND THE CIRCUIT CAN DIM THE LED.

CHALLENGES WITH BIGGER LOADS:

- **OSCILLATIONS:** WHEN SWITCHING LARGER LOADS, PARASITIC CAPACITANCE AND INDUCTANCE CAN CAUSE VOLTAGE SPIKES (UP TO 64V), POTENTIALLY DAMAGING THE MOSFET. THIS ISSUE CAN BE MITIGATED BY CONTROLLING THE GATE CURRENT.
- **SOLUTION:** USING A RESISTOR (E.G., 470 Ω) BETWEEN THE ARDUINO AND GATE SLOWS DOWN SWITCHING, REDUCING OSCILLATIONS AND IMPROVING STABILITY.

HIGH-FREQUENCY CONSIDERATIONS:

- AT HIGHER FREQUENCIES (E.G., 1MHz), GATE SWITCHING LOSSES BECOME NOTICEABLE. AT LOW FREQUENCIES (E.G., 490Hz), THEY ARE MINIMAL.

CONCLUSION:

MOSFETs IMPROVE CIRCUIT EFFICIENCY AND REDUCE HEAT LOSS, ESPECIALLY IN HIGH-POWER APPLICATIONS. HOWEVER, MANAGING GATE DRIVE AND OSCILLATIONS IS CRUCIAL FOR RELIABLE

PERFORMANCE. FOR DEMANDING APPLICATIONS, **MOSFET DRIVER ICs** CAN SIMPLIFY THE DESIGN AND REDUCE LOSSES.

40. USING BJTs AS SWITCHES

BJTs (NPN/PNP) ARE COMMONLY USED TO CONTROL LOADS. HERE'S A QUICK GUIDE:

1. NPN BJT SETUP:

- **CONNECT EMITTER TO GROUND, COLLECTOR TO LOAD, AND BASE TO CONTROL VOLTAGE VIA A CURRENT-LIMITING RESISTOR.**
- **THE BASE CURRENT IS CRITICAL AND MUST BE CALCULATED BASED ON THE CURRENT GAIN (B).**

2. ISSUES:

- **OVERDRIVING THE BASE CAN DAMAGE THE TRANSISTOR. ALWAYS USE A RESISTOR.**
- **LARGER LOADS MAY REQUIRE MORE BASE CURRENT FOR FULL SATURATION.**

3. LARGER LOADS:

- **FOR HIGHER CURRENTS, USE HIGHER-RATED TRANSISTORS (E.G., **BD 535** FOR UP TO **8A**).**

4. POWER LOSS:

- **BJTs CAN CREATE SIGNIFICANT HEAT AND POWER LOSS, ESPECIALLY WITH HIGH CURRENTS.**

5. SOLUTION - DARLINGTON TRANSISTORS:

- **USE DARLINGTON TRANSISTORS LIKE THE **TIP 142** FOR HIGHER CURRENT GAIN AND EASIER CONTROL WITH MICROCONTROLLERS.**

CONCLUSION: BJTs ARE GOOD FOR SWITCHING, BUT FOR HIGH-POWER APPLICATIONS, DARLINGTON TRANSISTORS ARE MORE EFFICIENT.

41. OP-AMP BASICS

OP-AMPS (OPERATIONAL AMPLIFIERS) ARE VERSATILE COMPONENTS USED IN BOTH ANALOG AND DIGITAL ELECTRONICS. HERE'S A QUICK BREAKDOWN:

1. OP-AMP SETUP:

- **COMMONLY AVAILABLE IN ICs WITH MULTIPLE OP-AMPS INSIDE (E.G., LM358).**
- **THE NON-INVERTING INPUT RECEIVES THE INPUT VOLTAGE, AND THE INVERTING INPUT GETS FEEDBACK FROM THE OUTPUT.**

2. OP-AMP GAIN:

- **THE GAIN OF THE OP-AMP IS DETERMINED BY THE RATIO OF RESISTORS IN A FEEDBACK LOOP. THE FORMULA FOR GAIN IS: $\text{GAIN} = \frac{R_2}{R_1} + 1$**
- **THIS IS USED TO AMPLIFY SIGNALS (E.G., FROM SENSORS OR MICROPHONES).**

3. ISSUES WITH VOLTAGE SWING:

- **THE OUTPUT VOLTAGE IS LIMITED BY THE SUPPLY VOLTAGE, SO YOU MAY NEED A DC OFFSET TO AMPLIFY AC SIGNALS LIKE AUDIO.**
- **RAIL-TO-RAIL OP-AMPS CAN OUTPUT CLOSE TO THE SUPPLY VOLTAGE, IMPROVING PERFORMANCE.**

4. INVERTING VS. NON-INVERTING:

- **INVERTING OP-AMPS PROVIDE A NEGATIVE GAIN, SUITABLE FOR AMPLIFYING AC SIGNALS WITHOUT AFFECTING DC.**
- **NON-INVERTING OP-AMPS AMPLIFY SIGNALS WITHOUT INVERSION.**

5. OP-AMP AS A COMPARATOR:

- **WHEN THERE'S NO FEEDBACK LOOP, THE OP-AMP BEHAVES AS A COMPARATOR, SWITCHING ITS OUTPUT BASED ON WHICH INPUT IS HIGHER.**

OP-AMPS ARE POWERFUL AND FLEXIBLE, USED FOR AMPLIFIERS, FILTERS, INTEGRATORS, DIFFERENTIATORS, AND MANY MORE APPLICATIONS IN ELECTRONICS!

42. THYRISTOR BASICS

A THYRISTOR IS A CONTROLLABLE DIODE THAT CAN BE TURNED ON AND OFF. UNLIKE REGULAR DIODES, WHICH ALLOW CURRENT TO FLOW ONLY IN ONE DIRECTION, A THYRISTOR HAS FOUR LAYERS AND THREE TERMINALS: ANODE, CATHODE, AND GATE. HERE'S A BREAKDOWN:

1. STRUCTURE AND FUNCTION:

- **A THYRISTOR CONSISTS OF FOUR SEMICONDUCTOR LAYERS AND HAS AN ADDITIONAL GATE TERMINAL TO CONTROL THE CURRENT FLOW.**
- **WHEN A POSITIVE VOLTAGE IS APPLIED TO THE GATE, IT TURNS ON, ALLOWING CURRENT TO FLOW BETWEEN THE ANODE AND CATHODE.**

2. LATCHING CURRENT:

- **A THYRISTOR STAYS CONDUCTIVE EVEN AFTER THE GATE SIGNAL IS REMOVED, PROVIDED THE CURRENT REMAINS ABOVE A CERTAIN LEVEL CALLED LATCHING CURRENT.**
- **ONCE THE CURRENT FALLS BELOW THE HOLDING CURRENT, IT TURNS OFF.**

3. APPLICATIONS AND ISSUES:

- **THYRISTORS ARE USED TO CONTROL THE FLOW OF POWER IN AC CIRCUITS, BUT THEY CANNOT EASILY TURN OFF WITHOUT CUTTING THE CURRENT (E.G., USING A MOSFET).**
- **IN AC CIRCUITS, A TRIAC (A THYRISTOR IN INVERSE PARALLEL CONFIGURATION) IS USED TO CONTROL BOTH HALVES OF THE WAVEFORM.**

4. AC CONTROL CIRCUIT:

- **A TRIAC AND OPTO-COUPLER COMBINATION CAN BE USED TO CREATE A PHASE ANGLE CONTROL CIRCUIT.**
- **THE MICROCONTROLLER (E.G., ARDUINO) DETECTS THE ZERO CROSSING POINT OF THE AC SIGNAL, DELAYS IT BASED ON A POTENTIOMETER INPUT, AND TRIGGERS THE TRIAC, CONTROLLING THE POWER DELIVERED TO THE LOAD (E.G., A LIGHT BULB).**

5. DISADVANTAGES:

- **THIS METHOD IS USEFUL FOR CONTROLLING POWER TO AC APPLIANCES OR MOTORS BUT HAS THE DOWNSIDE OF LOWERING THE POWER FACTOR DUE TO THE NON-SINUSOIDAL CURRENT WAVEFORM.**

IN CONCLUSION, WHILE THYRISTORS PROVIDE USEFUL CONTROL IN AC CIRCUITS, THEY HAVE LIMITATIONS THAT REQUIRE CAREFUL HANDLING, ESPECIALLY IN TERMS OF POWER FACTOR AND TURNING THEM OFF.

44. UNDERSTANDING BRUSHLESS DC MOTORS AND ESCs

IN THIS VIDEO, WE EXPLORE BRUSHLESS DC MOTORS (BLDC) AND HOW THEY WORK WITH AN ESC (ELECTRONIC SPEED CONTROLLER). HERE'S A BREAKDOWN:

DC MOTORS VS. BRUSHLESS MOTORS

- **DC MOTORS USE DIRECT CURRENT TO CREATE A ROTATIONAL MOVEMENT VIA A COMMUTATOR, WHICH SWITCHES THE DIRECTION OF CURRENT TO THE COILS, CAUSING THEM TO ROTATE.**
- **A BRUSHLESS MOTOR ALSO USES DIRECT CURRENT, BUT THE KEY DIFFERENCE IS THAT IT DOESN'T HAVE BRUSHES OR A COMMUTATOR. INSTEAD, IT USES PERMANENT MAGNETS ON THE ROTOR AND COILS ON THE STATOR, AND IT RELIES ON ELECTRONIC CONTROL TO CREATE A ROTATING MAGNETIC FIELD.**

BRUSHLESS MOTOR STRUCTURE

- **A BRUSHLESS MOTOR'S ROTOR CONSISTS OF PERMANENT MAGNETS, AND THE STATOR CONTAINS MULTIPLE COILS (WOUND IN A STAR OR DELTA CONFIGURATION).**
- **TO MAKE THE ROTOR SPIN, THE MOTOR ENERGIZES PAIRS OF COILS IN SEQUENCE, PRODUCING A ROTATING MAGNETIC FIELD THAT PULLS AND PUSHES THE ROTOR MAGNETS. THIS PROCESS IS CONTROLLED BY THE ESC.**

ESC (ELECTRONIC SPEED CONTROLLER)

- **THE ESC IS RESPONSIBLE FOR POWERING THE COILS IN THE STATOR. IT SWITCHES THE CURRENT TO THE COILS TO CREATE A ROTATING MAGNETIC FIELD, ENABLING THE ROTOR TO SPIN.**
- **THE ESC USES MOSFETs (METAL-OXIDE-SEMICONDUCTOR FIELD-EFFECT TRANSISTORS) TO SWITCH THE CURRENT BETWEEN HIGH, LOW, AND FLOATING STATES. THE NUMBER OF MOSFETs DETERMINES HOW MUCH CURRENT THE ESC CAN HANDLE, WHICH INFLUENCES THE POWER OUTPUT.**

- **BY ADJUSTING THE FREQUENCY OF THE CONTROL SIGNAL (I.E., HOW FAST THE COILS ARE ENERGIZED), THE ESC CONTROLS THE MOTOR'S SPEED AND RPM (REVOLUTIONS PER MINUTE).**

TORQUE AND RPM

- **TORQUE AND RPM ARE INVERSELY RELATED. A MOTOR WITH MORE MAGNETS AND COILS CAN ACHIEVE HIGHER TORQUE AT LOWER RPM, WHICH IS WHY OUTRUNNER BRUSHLESS MOTORS ARE FAVORED FOR HIGH-TORQUE APPLICATIONS LIKE ELECTRIC LONGBOARDS AND DRONES. THESE MOTORS HAVE MAGNETS PLACED ON THE OUTER PART OF THE ROTOR, GIVING THEM MORE SPACE FOR MAGNETS, RESULTING IN GREATER TORQUE.**
- **THE KV RATING (RPM PER VOLT APPLIED) DETERMINES HOW MANY RPMs THE MOTOR WILL ACHIEVE FOR EACH VOLT OF INPUT. HIGHER KV RATINGS RESULT IN HIGHER RPM BUT LOWER TORQUE.**

PRACTICAL EXAMPLE

- **WITH A 520 KV MOTOR:**
 - **AT 7.4V, IT REACHES 3,750 RPM.**
 - **AT 11.1V, IT REACHES 5,644 RPM.**
- **WITH A 920 KV MOTOR:**
 - **AT 7.4V, IT REACHES 6,780 RPM.**
 - **AT 11.1V, IT REACHES 10,500 RPM.**

THE HIGHER THE KV RATING, THE HIGHER THE POTENTIAL RPM, BUT WITH LOWER TORQUE. THE ESC ADJUSTS THE MOTOR SPEED BY CONTROLLING THE FREQUENCY OF THE SIGNALS SENT TO THE COILS.

CONCLUSION

BRUSHLESS MOTORS AND ESCs ARE ESSENTIAL IN APPLICATIONS WHERE HIGH EFFICIENCY, LOW MAINTENANCE, AND HIGH POWER ARE NEEDED, LIKE ELECTRIC LONGBOARDS, QUADCOPTERS, AND HARD DRIVES. BY UNDERSTANDING HOW THESE COMPONENTS WORK TOGETHER, YOU CAN DESIGN AND OPTIMIZE SYSTEMS FOR DIFFERENT POWER NEEDS AND PERFORMANCE GOALS.

45. UNDERSTANDING OSCILLATORS AND HOW THEY WORK

IN THIS VIDEO, WE EXPLORE OSCILLATORS, WHICH ARE CIRCUITS THAT GENERATE PERIODIC ALTERNATING SIGNALS LIKE SQUARE, TRIANGLE, OR SINE WAVES. THESE SIGNALS ARE CRUCIAL FOR TIMING IN DEVICES LIKE MICROCONTROLLERS, RADIOS, AND MULTIMETERS. LET'S DIVE INTO SOME OF THE MOST POPULAR TYPES OF OSCILLATORS AND HOW THEY WORK.

RELAXATION OSCILLATORS (RC CIRCUITS)

THE RELAXATION OSCILLATOR IS ONE OF THE SIMPLEST OSCILLATOR DESIGNS, AND IT OFTEN USES RC (RESISTOR-CAPACITOR) COMPONENTS. A CLASSIC EXAMPLE IS THE ASTABLE MULTIVIBRATOR:

- **TWO CAPACITORS (C1 AND C2) ARE CHARGED AND DISCHARGED ALTERNATELY THROUGH RESISTORS. THE TRANSISTORS IN THE CIRCUIT SWITCH BETWEEN ON AND OFF STATES BASED ON THE CAPACITOR VOLTAGES.**
- **WHEN THE VOLTAGE ACROSS A CAPACITOR HITS A CERTAIN THRESHOLD, THE TRANSISTOR SWITCHES, DISCHARGING THE CAPACITOR AND CHARGING THE OTHER ONE. THIS CREATES A SQUARE WAVEFORM.**
- **IF YOU CHANGE THE RESISTANCE OR CAPACITANCE, YOU CAN INCREASE OR DECREASE THE FREQUENCY OF THE WAVEFORM. LOWERING RESISTANCE OR CAPACITANCE MAKES THE CYCLE FASTER, RESULTING IN A HIGHER FREQUENCY.**

555 TIMER OSCILLATOR

A 555 TIMER IC IS ANOTHER POPULAR WAY TO CREATE OSCILLATORS. IT WORKS BY CHARGING AND DISCHARGING A CAPACITOR USING INTERNAL COMPARATORS AND FLIP-FLOPS:

- **BY ADDING COMPONENTS LIKE A CAPACITOR, RESISTOR, AND POTENTIOMETER, YOU CAN CREATE A STABLE, VARIABLE SQUARE WAVE OUTPUT.**
- **THE THRESHOLD VOLTAGES (66% AND 33% OF THE SUPPLY VOLTAGE) ARE SET INTERNALLY, AND ADJUSTING THE EXTERNAL RESISTOR AND CAPACITOR VALUES CAN CHANGE THE FREQUENCY OF OSCILLATION.**

WHILE THESE CIRCUITS ARE SIMPLE AND EASY TO USE, THERE IS A LIMIT TO HOW HIGH THE FREQUENCY CAN GO BEFORE THE SIGNAL BECOMES TOO UNSTABLE OR HARD TO VIEW.

LC RESONATORS AND TANK CIRCUITS

WHEN HIGHER FREQUENCIES ARE NEEDED, LC RESONATORS (ALSO KNOWN AS TANK CIRCUITS) ARE USED:

- **THESE CONSIST OF A CAPACITOR AND AN INDUCTOR, WHICH STORE ELECTROSTATIC AND MAGNETIC ENERGY, RESPECTIVELY.**
- **THE CAPACITOR CHARGES AND DISCHARGES, TRANSFERRING ENERGY TO THE INDUCTOR, WHICH THEN DISCHARGES AND CHARGES THE CAPACITOR BACK. THIS PROCESS CREATES A SINE WAVE OF VOLTAGE AND CURRENT.**
- **THE FREQUENCY OF OSCILLATION IS DETERMINED BY THE RESONANT FREQUENCY, WHERE THE INDUCTANCE AND CAPACITANCE CANCEL OUT THE REACTANCES. AT THIS FREQUENCY, THE ENERGY TRANSFER BETWEEN THE CAPACITOR AND INDUCTOR IS VERY EFFICIENT.**

HOWEVER, OSCILLATION IN A PURE LC CIRCUIT WON'T LAST INDEFINITELY BECAUSE PARASITIC RESISTANCE (LIKE WIRE RESISTANCE) DISSIPATES ENERGY AS HEAT. TO SUSTAIN THE OSCILLATION, WE NEED TO AMPLIFY THE SIGNAL.

AMPLIFYING LC OSCILLATIONS

TO MAINTAIN THE OSCILLATION, YOU CAN USE AN AMPLIFIER, SUCH AS AN NPN TRANSISTOR, TO FEED ENERGY BACK INTO THE CIRCUIT AT THE RIGHT TIME. BY TUNING THE AMPLIFICATION FACTOR PROPERLY, YOU CAN CREATE A STABLE OSCILLATION, LIKE A HIGH-FREQUENCY SINE WAVE IN THE MEGAHERTZ RANGE.

CRYSTAL OSCILLATORS

FOR EVEN GREATER STABILITY, CRYSTAL OSCILLATORS ARE USED. THESE USE PIEZOELECTRIC CRYSTALS (SUCH AS QUARTZ) TO CREATE HIGHLY STABLE OSCILLATIONS AT A SPECIFIC FREQUENCY, LIKE 16 MHz:

- **THE CRYSTAL'S MECHANICAL VIBRATIONS ARE USED TO GENERATE A CONSISTENT OSCILLATING SIGNAL. THIS IS SIMILAR TO AN LC RESONATOR, BUT THE CRYSTAL PROVIDES VERY PRECISE FREQUENCY CONTROL.**
- **THESE OSCILLATORS ARE COMMONLY USED IN MICROCONTROLLERS TO SET THE CLOCK SPEED AND ENSURE STABLE TIMING.**

CONCLUSION

OSCILLATORS ARE ESSENTIAL FOR GENERATING PERIODIC SIGNALS IN MANY ELECTRONIC APPLICATIONS, FROM MICROCONTROLLERS TO RADIO COMMUNICATION. WHETHER USING SIMPLE RC CIRCUITS, ADVANCED LC RESONATORS, OR HIGHLY PRECISE CRYSTAL OSCILLATORS, THEY ALLOW DEVICES TO KEEP TIME AND SYNCHRONIZE OPERATIONS.

46. "Essential Applications of Resistors in Electronic Circuits"

RESISTORS ARE ESSENTIAL COMPONENTS IN ELECTRONIC CIRCUITS, USED TO CONTROL CURRENT, DIVIDE VOLTAGES, AND PROTECT OTHER COMPONENTS. THEIR PRIMARY FUNCTION IS TO LIMIT THE CURRENT, FOR EXAMPLE, BY CONNECTING A LED TO A POWER SOURCE. THE OHM'S LAW IS USED TO CALCULATE THE PROPER RESISTANCE VALUE.

RESISTORS CAN ALSO BE USED AS VOLTAGE DIVIDERS TO CREATE LOWER VOLTAGES, WHICH IS USEFUL FOR CONNECTING MODULES LIKE THE ESP8266. POTENTIOMETERS ALLOW YOU TO ADJUST THE INPUT VOLTAGE IN CIRCUITS.

IN ADDITION, RESISTORS ARE USED FOR STABILIZING INPUTS WITH PULL-UP AND PULL-DOWN RESISTANCES, MEASURING CURRENT THROUGH SHUNT RESISTORS, AND ACTING AS FUSES TO PROTECT CIRCUITS.

IN ALTERNATING CURRENT (AC) CIRCUITS, RESISTORS WORK SIMILARLY TO DIRECT CURRENT (DC) CIRCUITS, BUT WITH PARASITIC EFFECTS LIKE CAPACITIVE REACTANCE THAT INFLUENCE CURRENT AT HIGH FREQUENCIES.

47. TEMPERATURE MEASUREMENT AND THERMOMETER BUILDING:

- **NTC THERMISTORS: RESISTANCE DECREASES AS TEMPERATURE RISES, BUT THEY HAVE NON-LINEAR CHARACTERISTICS AND ARE LIMITED IN RANGE (UP TO 150°C).**
- **PT100 SENSORS: OFFER MORE ACCURATE, LINEAR MEASUREMENTS AND ARE IDEAL FOR HIGHER TEMPERATURES (UP TO 850°C).**
- **MEASUREMENT METHODS: USE CONSTANT CURRENT AND OHM'S LAW, OR A WHEATSTONE BRIDGE FOR BETTER ACCURACY AND TO ELIMINATE OFFSET VOLTAGE.**
- **CHALLENGES: VOLTAGE OFFSETS AND LOW RESOLUTION CAN AFFECT ACCURACY; SOLUTIONS INCLUDE DIFFERENTIAL AMPLIFIERS OR PRE-MADE TRANSMITTERS.**
- **ALTERNATIVE SENSORS: LM35 PROVIDES A LINEAR OUTPUT FROM 2°C TO 150°C, WHILE DS18B20 OFFERS DIGITAL OUTPUT WITH GOOD ACCURACY.**
- **PROTOTYPING: MICROCONTROLLERS AND AN LCD CAN DISPLAY TEMPERATURE AFTER SIGNAL PROCESSING.**

49. INDUCTANCE AND REACTANCE:

- **INDUCTIVE REACTANCE:** INDUCTORS CREATE REACTANCE, WHICH BEHAVES LIKE RESISTANCE BUT STORES ENERGY IN A MAGNETIC FIELD INSTEAD OF CONVERTING IT INTO HEAT. THIS CAUSES A PHASE SHIFT BETWEEN VOLTAGE AND CURRENT.
- **CURRENT AND FREQUENCY:** INCREASING FREQUENCY INCREASES THE INDUCTIVE REACTANCE, REDUCING CURRENT FLOW THROUGH THE CIRCUIT. THE FORMULA FOR INDUCTIVE REACTANCE IS $X_L = 2\pi fL$, WHERE f IS THE FREQUENCY AND L IS INDUCTANCE.
- **REACTANCE AND POWER:** INDUCTIVE REACTANCE CAN CAUSE OSCILLATING POWER BETWEEN THE VOLTAGE SOURCE AND THE LOAD, WHICH IS CALLED REACTIVE POWER, AFFECTING POWER GRIDS.
- **PHASE SHIFT:** INDUCTIVE CIRCUITS CAN HAVE A PHASE SHIFT, WHICH CAN BE USED TO MEASURE INDUCTANCE OR ANALYZE POWER GRIDS. THE PHASE SHIFT CAN REACH 90° FOR AN IDEAL INDUCTOR.
- **PRACTICAL USE:** INDUCTORS CAN BE USED FOR NOISE FILTERS (HIGH-PASS AND LOW-PASS FILTERS) IN AUDIO OR SIGNAL PROCESSING APPLICATIONS. PHASE SHIFT CAN INDICATE INDUCTANCE IN DEVICES LIKE MICROWAVE MOTORS.
- **MEASURING INDUCTANCE:** A TRANSISTOR TESTER, AVAILABLE FOR AROUND \$20, CAN MEASURE INDUCTANCE, RESISTANCE, AND CAPACITANCE, THOUGH IT MAY LACK THE RESOLUTION FOR SMALLER INDUCTORS.

IN CONCLUSION, INDUCTORS PLAY A CRUCIAL ROLE IN REACTIVE POWER, PHASE SHIFTS, AND FILTERING APPLICATIONS, WITH PRACTICAL TOOLS AVAILABLE FOR MEASURING THEIR PROPERTIES.

50. INDUCTORS AND THEIR IMPORTANCE IN ELECTRONICS:

- **INDUCTORS IN EVERYDAY DEVICES:** INDUCTORS (OR COILS) ARE COMMON IN VARIOUS ELECTRONICS, INCLUDING MOTORS, TRANSFORMERS, AND RELAYS. THEY ARE ESSENTIAL FOR CREATING MAGNETIC FIELDS WHEN CURRENT FLOWS THROUGH THEM.
- **BASIC PRINCIPLE:** WHEN CURRENT FLOWS THROUGH A WIRE, IT GENERATES A MAGNETIC FIELD AROUND IT. INCREASING THE CURRENT INCREASES THE STRENGTH OF THIS FIELD. BY WINDING THE WIRE, YOU CAN AMPLIFY THE MAGNETIC FIELD, AND USING A FERROMAGNETIC CORE (LIKE IRON) ENHANCES IT EVEN MORE, CREATING AN ELECTROMAGNET.

- **INDUCTANCE:** THE PROPERTY OF A COIL TO CREATE A MAGNETIC FIELD IS CALLED INDUCTANCE, MEASURED IN HENRYS (H). INDUCTANCE CAN BE MEASURED WITH AN RLC METER OR CALCULATED THROUGH DIFFERENT METHODS.
- **COILS IN DC CIRCUITS:** IN DC CIRCUITS, COILS RESIST CHANGES IN CURRENT FLOW. THIS IS DUE TO LENZ'S LAW, WHICH STATES THAT THE INDUCED CURRENT IN A COIL OPPOSES THE CHANGE IN THE CIRCUIT. AS A RESULT, THE CURRENT TAKES TIME TO REACH ITS STEADY STATE.
- **ENERGY STORAGE:** THE ENERGY STORED IN A COIL IS PROPORTIONAL TO ITS INDUCTANCE AND THE SQUARE OF THE CURRENT. THIS ENERGY CAN BE USED IN APPLICATIONS LIKE BOOST CONVERTERS TO STEP UP VOLTAGE (E.G., FROM 3.7V TO 5V).
- **SWITCHING AND PROTECTION:** WHEN USING COILS IN SWITCHING CIRCUITS (E.G., FOR MOTORS OR CONVERTERS), INDUCTORS CAN GENERATE VOLTAGE SPIKES WHEN THE SWITCH OPENS. TO PREVENT DAMAGE, FLYBACK DIODES ARE USED TO PROVIDE A PATH FOR THE CURRENT, PROTECTING THE SWITCH.
- **NEXT STEPS:** IN PART 2, WE WILL EXPLORE HOW INDUCTORS BEHAVE IN AC CIRCUITS, INCLUDING THEIR REACTANCE AND THEIR USE IN FREQUENCY FILTERS.

INDUCTORS PLAY A VITAL ROLE IN ENERGY STORAGE, VOLTAGE REGULATION, AND CURRENT REGULATION IN BOTH DC AND AC CIRCUITS.

51. HANDLING THE TC35 GSM MODULE AND SENDING SMS:

- **INTRODUCTION TO THE TC35 GSM MODULE:** THE TC35 GSM MODULE IS A RELATIVELY AFFORDABLE DEVICE THAT ALLOWS YOU TO SEND SMS MESSAGES VIA A MICROCONTROLLER LIKE THE ARDUINO UNO. IT'S AVAILABLE FOR AROUND \$23 ON PLATFORMS LIKE EBAY, WITH SOME EVEN CHEAPER OPTIONS.
- **SETTING UP THE MODULE:**
 - **SIM CARD:** INSERT A PREPAID SIM CARD INTO THE MODULE'S CARD HOLDER. IT'S RECOMMENDED TO FIRST USE A SMARTPHONE TO REMOVE THE SIM LOCK BEFORE PLACING THE CARD INTO THE MODULE.
 - **POWER SUPPLY:** POWER THE MODULE WITH 5V (DC JACK OR VCC AND GROUND PINS). AVOID USING VOLTAGES HIGHER THAN 6V TO PROTECT THE MAX 232 IC. IF USING 12V, REMOVE THE MAX 232 CHIP TO AVOID DAMAGE.

- **LOGIN PROCESS:** THE MODULE REQUIRES A LOGIN PROCESS TO THE MOBILE NETWORK, INITIATED BY A BUTTON ON THE BOARD. FOR AUTOMATION, A JUMPER WIRE CAN BE ADDED TO TRIGGER THE LOGIN PROCESS VIA A MICROCONTROLLER (E.G., ARDUINO) BY CONNECTING IT TO PIN 10. WHEN THE LED BLINKS EVERY 2-3 SECONDS, THE MODULE IS SUCCESSFULLY CONNECTED.
- **TESTING WITH FTDI BREAKOUT:**
 - **WIRING:** CONNECT THE FTDI BREAKOUT TO THE TC35 GSM MODULE USING THE FOLLOWING CONNECTIONS: TX TO RXD0, RX TO TXD0, AND GROUND TO GROUND. DESPITE THE GSM MODULE USING 3.3V LOGIC, IT IS COMPATIBLE WITH 5V SIGNALS FROM THE FTDI AND ARDUINO.
 - **SERIAL COMMUNICATION:** USE AT COMMANDS TO COMMUNICATE WITH THE MODULE. FOR EXAMPLE, TYPING "A" RETURNS "OK," CONFIRMING THE CONNECTION. YOU CAN ALSO CHECK NETWORK DETAILS LIKE SIGNAL STRENGTH.
- **ARDUINO INTEGRATION:**
 - **WIRING:** CONNECT THE TC35 MODULE TO THE ARDUINO UNO, USING PIN 10 TO INITIATE THE LOGIN PROCESS (INSTEAD OF THE MANUAL BUTTON). THIS WIRING SETUP SIMPLIFIES AUTOMATION.
 - **SENDING SMS:** THE ARDUINO SKETCH HANDLES THE PROCESS OF SENDING AN SMS. ENTER THE DESIRED PHONE NUMBER AND MESSAGE IN THE CODE, FINISH THE MESSAGE WITH A DOT, AND THE ARDUINO SENDS THE SMS AUTOMATICALLY. THE PHONE NUMBER SHOULD BE IN INTERNATIONAL FORMAT (E.G., +49 FOR GERMANY).
- **FUTURE PROJECTS:** THIS SETUP CAN BE USED FOR MORE COMPLEX APPLICATIONS, SUCH AS BUILDING AN ALARM SYSTEM THAT SENDS SMS NOTIFICATIONS.

CONCLUSION: THE TC35 GSM MODULE IS A VERSATILE AND EASY-TO-USE DEVICE FOR SENDING SMS MESSAGES VIA A MICROCONTROLLER. WITH SIMPLE WIRING AND AT COMMANDS, IT CAN BE INTEGRATED INTO VARIOUS DIY PROJECTS.

52. DIGITAL-TO-ANALOG CONVERTERS (DAC) AND ARDUINO:

- **INTRODUCTION TO DAC:**
A DIGITAL-TO-ANALOG CONVERTER (DAC) TAKES A DIGITAL INPUT AND CONVERTS IT INTO AN ANALOG OUTPUT. THE DIGITAL INPUT IS TYPICALLY A SERIES OF BITS (1S AND 0S), AND THE DAC TRANSFORMS THESE INTO A CONTINUOUS VOLTAGE SIGNAL. THIS IS ESSENTIAL IN

VARIOUS APPLICATIONS LIKE AUDIO SYSTEMS, WHERE YOU NEED TO CONVERT DIGITAL AUDIO DATA TO AN ANALOG AUDIO SIGNAL.

- **RESISTOR LADDER DAC:**

ONE SIMPLE WAY TO BUILD A **DAC** IS USING A RESISTOR LADDER. IN THIS SETUP, YOU USE RESISTORS TO CREATE A VOLTAGE DIVIDER, WHICH IS CONTROLLED BY DIGITAL PINS FROM A MICROCONTROLLER (LIKE ARDUINO). EACH BIT OF THE DIGITAL SIGNAL CORRESPONDS TO A RESISTOR'S POSITION, WHICH CONTROLS THE VOLTAGE OUTPUT.

- **EXAMPLE: WITH 10kΩ AND 20kΩ RESISTORS, YOU CAN SET THE OUTPUT VOLTAGE DEPENDING ON THE DIGITAL SIGNAL'S STATE. FOR EXAMPLE, SETTING PIN 7 HIGH AND OTHERS LOW GIVES A SPECIFIC OUTPUT VOLTAGE, CORRESPONDING TO THE BINARY INPUT.**

- **VOLTAGE OUTPUT EXPERIMENTATION:**

BY CHANGING THE DIGITAL INPUT VALUES FROM 0 TO 255 (FOR AN 8-BIT **DAC**), YOU CAN CONTROL THE OUTPUT VOLTAGE. FOR EXAMPLE, ENTERING THE NUMBER 12 (HALF OF 256) GIVES HALF OF THE MAX OUTPUT VOLTAGE (AROUND 2.3V). THIS ISN'T PERFECTLY PRECISE DUE TO RESISTOR TOLERANCES, BUT IT DEMONSTRATES THE BASIC CONCEPT.

- **WAVEFORMS:**

WITH THE **DAC** SET UP, YOU CAN GENERATE DIFFERENT WAVEFORMS:

- **RAMP FUNCTION: BY GRADUALLY INCREASING THE DIGITAL INPUT, YOU CAN CREATE A RAMP FUNCTION, AND BY DECREASING IT, A REVERSE RAMP.**
- **TRIANGLE WAVE: BY CONTINUOUSLY INCREASING AND THEN DECREASING THE DIGITAL INPUT, YOU CAN CREATE A TRIANGLE WAVE.**
- **SINE WAVE: FOR SOUND GENERATION, YOU CAN CREATE A SINE WAVE USING THIS **DAC** SETUP, BUT TO DRIVE A SPEAKER, AN AMPLIFIER IS NECESSARY TO MAINTAIN STABLE OUTPUT VOLTAGE.**

- **USING ARDUINO'S BUILT-IN PWM:**

THE ARDUINO HAS A BUILT-IN FUNCTION CALLED `analogWrite()`, WHICH CAN OUTPUT A PULSE WIDTH MODULATION (**PWM**) SIGNAL. **PWM** SIMULATES AN ANALOG SIGNAL BY RAPIDLY SWITCHING THE OUTPUT BETWEEN HIGH AND LOW STATES. FOR EXAMPLE, A **PWM** SIGNAL WITH A DUTY CYCLE OF 78.4% WOULD RESULT IN AN AVERAGE VOLTAGE OF AROUND 3.8V (BASED ON THE DUTY CYCLE).

- **LOW-PASS FILTERING: TO SMOOTH OUT THE **PWM** SIGNAL INTO A MORE CONTINUOUS VOLTAGE, A LOW-PASS FILTER (USING A RESISTOR AND CAPACITOR)**

CAN BE ADDED. THIS REMOVES THE HIGH-FREQUENCY SWITCHING AND GIVES A CLEANER ANALOG OUTPUT.

- **EXTERNAL DAC ICs:**

IF YOU NEED A MORE PRECISE AND COMPACT **DAC**, YOU CAN LOOK INTO USING SPECIALIZED **DAC ICs** LIKE THE **DAC0800** OR THE **MCP4725 (12-BIT DAC)**. THESE **ICs** SIMPLIFY THE PROCESS AND OFFER HIGHER PRECISION FOR YOUR ANALOG OUTPUT NEEDS.

- **PCF8591 DAC:**

ANOTHER AFFORDABLE OPTION IS THE **PCF8591**, A 4-BIT **DAC** THAT WORKS WELL FOR PROJECTS REQUIRING BASIC ANALOG OUTPUT. IT USES **I2C** COMMUNICATION, ALLOWING EASY INTEGRATION WITH MICROCONTROLLERS LIKE **ARDUINO**.

- **CONCLUSION:**

WHILE **ARDUINO's PWM** CAN MIMIC ANALOG SIGNALS, USING A PROPER **DAC** GIVES YOU SMOOTHER, MORE ACCURATE ANALOG SIGNALS. FOR MORE ADVANCED APPLICATIONS LIKE AUDIO OR VIDEO FREQUENCY GENERATION, A **DAC** WITH HIGHER RESOLUTION, LIKE THE **MCP4725**, IS HIGHLY RECOMMENDED.

FUTURE PROJECTS:

THE VIDEO SUGGESTS UPCOMING PROJECTS THAT WILL INVOLVE AUDIO AND VIDEO FREQUENCY GENERATION, AUDIO FILTERS, AND POSSIBLY MORE **DAC**-BASED PROJECTS.

CONCLUSION:

DACs ARE ESSENTIAL FOR CONVERTING DIGITAL SIGNALS INTO ANALOG OUTPUTS, ESPECIALLY IN AUDIO APPLICATIONS. SIMPLE RESISTOR LADDERS, **ARDUINO's PWM**, OR DEDICATED **DAC ICs** LIKE THE **PCF8591** OR **MCP4725** OFFER VARYING LEVELS OF PRECISION AND EASE OF USE, DEPENDING ON THE PROJECT'S NEEDS.

53. INTRODUCTION TO DIODES AND THEIR IMPORTANCE IN CIRCUITS

DIODES ARE ONE OF THE MOST FUNDAMENTAL ELECTRONIC COMPONENTS, AND THEY'RE USED IN NEARLY EVERY POWER SUPPLY AND ELECTRONIC DEVICE. YOU CAN FIND DIODES IN BOTH OLD LINEAR POWER SUPPLIES (TYPICALLY IN FOUR UNITS) AND NEWER SWITCHING POWER SUPPLIES. EVEN IN SMALL ELECTRONICS LIKE A **BANANA PI**, YOU CAN SPOT **SMD (SURFACE-MOUNT DEVICE)** DIODES. BUT WHY ARE DIODES SO CRITICAL, AND HOW DO THEY FUNCTION IN CIRCUITS? LET'S BREAK IT DOWN:

HOW DIODES WORK IN DC CIRCUITS

A DIODE IS A SEMICONDUCTOR DEVICE THAT ALLOWS CURRENT TO FLOW ONLY IN ONE DIRECTION. IN A DC CIRCUIT WHERE CURRENT FLOWS IN A SINGLE DIRECTION (LIKE IN AN LED BLINK CIRCUIT), A DIODE PLAYS AN IMPORTANT ROLE IN ENSURING THAT THE CIRCUIT OPERATES SAFELY.

1. NORMAL OPERATION (CORRECT POLARITY):

IN A BASIC CIRCUIT WITH AN LED, IF YOU CONNECT 5V TO THE POSITIVE TERMINAL AND GROUND TO THE OTHER TERMINAL, THE CURRENT FLOWS NORMALLY, AND THE LED BLINKS. THIS WORKS BECAUSE THE CURRENT FLOWS FROM THE POSITIVE TERMINAL TO THE NEGATIVE, AS EXPECTED.

2. REVERSE POLARITY (INCORRECT POWER CONNECTION):

IF YOU ACCIDENTALLY REVERSE THE POWER CONNECTIONS, THE CIRCUIT WILL LIKELY BE DESTROYED UNLESS YOU HAVE A DIODE IN PLACE. BY PLACING THE DIODE IN SERIES WITH THE CIRCUIT, IT WILL BLOCK CURRENT FLOW WHEN THE POLARITY IS REVERSED. THIS ENSURES THAT NO CURRENT FLOWS WHEN THE POWER IS CONNECTED THE WRONG WAY, PREVENTING DAMAGE TO THE CIRCUIT.

UNDERSTANDING DIODE'S VOLTAGE DROP

EVEN THOUGH DIODES BLOCK REVERSE CURRENT, THEY HAVE A SMALL VOLTAGE DROP WHEN FORWARD-BIASED (I.E., WHEN THEY ALLOW CURRENT TO FLOW). FOR EXAMPLE, IF YOU'RE USING A 1N4007 DIODE, YOU MIGHT NOTICE A VOLTAGE DROP OF AROUND 0.7V WHEN CURRENT IS FLOWING THROUGH THE DIODE. THIS MEANS THAT IN A 5V SYSTEM, AFTER THE DIODE, THE CIRCUIT MIGHT ONLY GET AROUND 4.35V INSTEAD OF THE FULL 5V.

- **POWER LOSS:**

THIS VOLTAGE DROP LEADS TO SOME POWER LOSS, WHICH MIGHT SEEM MINIMAL IN LOW-CURRENT CIRCUITS, BUT IN HIGH-CURRENT CIRCUITS, IT COULD CAUSE THE DIODE TO HEAT UP AND REQUIRE A LARGER, HIGHER-POWER DIODE TO HANDLE THE LOAD.

DIODES IN AC-TO-DC CONVERSION

DIODES ARE VERY USEFUL IN CONVERTING AC (ALTERNATING CURRENT) TO DC (DIRECT CURRENT). LET'S LOOK AT HOW DIODES ACHIEVE THIS:

1. AC SOURCE:

IF YOU HAVE AN AC SIGNAL, LIKE FROM A 220V TO 15V TRANSFORMER, THE SIGNAL OSCILLATES BETWEEN POSITIVE AND NEGATIVE VOLTAGES. THIS IS A SINE WAVE, AND ITS VOLTAGE FLUCTUATES BETWEEN MAXIMUM AND MINIMUM VALUES.

- THE RMS VALUE (ROOT MEAN SQUARE) IS TYPICALLY USED TO REPRESENT THE AVERAGE VOLTAGE OF AN AC SIGNAL. IN THIS CASE, THE TRANSFORMER MIGHT SAY IT

PROVIDES **15V RMS**, BUT THE PEAK VOLTAGE (MAX VOLTAGE) IS ACTUALLY HIGHER, AROUND **18V**. THIS IS BECAUSE THE **RMS** VALUE IS ALWAYS LOWER THAN THE PEAK VALUE FOR SINE WAVES.

2. HALF-WAVE RECTIFICATION:

BY ADDING A SINGLE DIODE TO THE **AC** SIGNAL, YOU CAN "RECTIFY" IT, MEANING YOU ONLY GET THE POSITIVE HALF OF THE WAVE. THIS IS CALLED HALF-WAVE RECTIFICATION, BUT THE RESULT IS A BUMPY **DC** SIGNAL—ONLY POSITIVE VOLTAGE, BUT WITH A FLUCTUATING PATTERN.

- TO SMOOTH THE OUTPUT AND REDUCE THE BUMPS, A CAPACITOR IS ADDED. THE CAPACITOR CHARGES UP DURING THE PEAKS OF THE VOLTAGE AND DISCHARGES DURING THE DIPS, MAKING THE OUTPUT **DC** LESS BUMPY. HOWEVER, THIS STILL ISN'T PERFECT BECAUSE IT CAN'T CHARGE UP IMMEDIATELY ON EVERY CYCLE.

BRIDGE RECTIFIER FOR BETTER DC

TO IMPROVE THE RECTIFIED **DC** SIGNAL, YOU CAN USE A BRIDGE RECTIFIER, WHICH IS ESSENTIALLY FOUR DIODES ARRANGED IN A SPECIFIC CONFIGURATION. THIS ALLOWS BOTH THE POSITIVE AND NEGATIVE CYCLES OF THE **AC** INPUT TO BE CONVERTED INTO POSITIVE **DC**.

- **How It Works:**

IN THE BRIDGE RECTIFIER, NO MATTER WHICH DIRECTION THE CURRENT FLOWS IN THE INPUT, IT WILL ALWAYS PASS THROUGH THE DIODES IN SUCH A WAY THAT ONLY POSITIVE CURRENT FLOWS THROUGH THE OUTPUT. THIS IS ACHIEVED BY ARRANGING THE DIODES SO THAT BOTH HALVES OF THE **AC** WAVEFORM ARE CONVERTED INTO POSITIVE VOLTAGE.

- **IMPROVED OUTPUT:**

THIS RESULTS IN MUCH SMOOTHER AND MORE CONSISTENT **DC**, WHICH IS IDEAL FOR POWERING ELECTRONIC DEVICES OR OTHER CIRCUITS.

CONCLUSION AND NEXT STEPS

THIS VIDEO GAVE A SOLID INTRODUCTION TO DIODES, SHOWING HOW THEY CAN PROTECT CIRCUITS FROM REVERSE POLARITY, HOW THEY ARE USED IN RECTIFYING **AC** SIGNALS INTO **DC**, AND THEIR VOLTAGE DROP AND EFFICIENCY CONSIDERATIONS.

WHILE THIS VIDEO COVERED BASIC RECTIFICATION AND HALF-WAVE AND BRIDGE RECTIFICATION, THERE ARE MANY MORE TYPES OF DIODES (LIKE **ZENER** DIODES, **LEDs**, AND **SCHOTTKY** DIODES) THAT HAVE SPECIAL FUNCTIONS.

IN THE FUTURE, YOU COULD EXPLORE MORE DIODE TYPES AND THEIR APPLICATIONS, INCLUDING VOLTAGE REGULATION OR USING DIODES FOR SIGNAL MODULATION IN DIFFERENT PROJECTS.

54. INTRODUCTION TO PROPER LED HANDLING AND USAGE

LEDs ARE AMONG THE MOST COMMON AND VERSATILE COMPONENTS IN ELECTRONICS, BUT AS SIMPLE AS THEY MAY SEEM, THERE ARE A LOT OF IMPORTANT DETAILS WHEN IT COMES TO USING THEM PROPERLY. IN THIS VIDEO, WE'LL GO THROUGH THE BASICS AND SOME ADVANCED TECHNIQUES FOR DRIVING LEDs THE RIGHT WAY.

BASIC LED CIRCUIT

WHEN YOU BUY LEDs FROM STORES LIKE AMAZON OR EBAY, YOU'LL USUALLY FIND TWO KEY PARAMETERS:

1. FORWARD VOLTAGE (TYPICALLY AROUND 3.2V)
2. CURRENT REQUIRED (USUALLY 20mA FOR STANDARD LEDs)

LET'S SAY YOU HAVE A 9V BATTERY AS YOUR POWER SOURCE. THE BASIC LED CIRCUIT WOULD LOOK SOMETHING LIKE THIS:

- POWER SOURCE: 9V
- LED FORWARD VOLTAGE: 3.2V
- REQUIRED CURRENT: 20mA

IF YOU CONNECT THE LED DIRECTLY TO THE POWER SOURCE WITHOUT A RESISTOR, THE LED WILL BURN OUT QUICKLY. WHY? BECAUSE WITHOUT A RESISTOR, THE LED DRAWS MORE CURRENT THAN IT CAN HANDLE, WHICH CAUSES IT TO OVERHEAT AND FAIL. SO, HOW DO WE CALCULATE THE PROPER RESISTOR VALUE?

CALCULATING RESISTOR VALUE

USING OHM'S LAW, WE CAN CALCULATE THE APPROPRIATE RESISTANCE:

$$R = \frac{V_{\text{SOURCE}} - V_{\text{LED}}}{I}$$

WHERE:

- $V_{\text{SOURCE}} = 9\text{V}$ (BATTERY VOLTAGE)
- $V_{\text{LED}} = 3.2\text{V}$ (LED FORWARD VOLTAGE)
- $I = 0.02\text{A}$ (20mA)

THE VOLTAGE DROP ACROSS THE RESISTOR NEEDS TO BE $9\text{V} - 3.2\text{V} = 5.8\text{V}$

USING OHM'S LAW:

$$R = 5.8V / 0.02A = 290 \Omega \quad R = \frac{5.8V}{0.02A} = 290 \, \Omega$$

YOU CAN USE A **290Ω** RESISTOR OR COMBINE TWO **150Ω** RESISTORS IN SERIES TO GET A SIMILAR RESULT. USING A LARGER RESISTOR LIKE **300Ω** WILL ALSO WORK.

RESISTOR POWER RATING

THE POWER DISSIPATED BY THE RESISTOR CAN BE CALCULATED USING:

$$P = V_{\text{RESISTOR}} \times I = 5.8V \times 0.02A = 0.116W \quad P = V_{\text{RESISTOR}} \times I = 5.8V \times 0.02A = 0.116W$$

SINCE A TYPICAL RESISTOR CAN HANDLE **0.25W**, A QUARTER-WATT RESISTOR IS SUFFICIENT FOR THIS CASE. BUT, IF THE RESISTOR IS OVERLOADED, IT COULD OVERHEAT, AS SHOWN IN THE VIDEO. SO BE SURE TO CHOOSE A RESISTOR WITH A SUFFICIENT POWER RATING.

SERIES VS. PARALLEL LEDs

NOW, LET'S CONSIDER CONNECTING TWO LEDs. IF YOU WERE TO PUT THEM IN PARALLEL, YOU'D NEED A SEPARATE RESISTOR FOR EACH LED, WHICH WASTES POWER. A BETTER APPROACH IS TO CONNECT THEM IN SERIES, WHICH KEEPS THE CURRENT THE SAME THROUGH BOTH LEDs AND REDUCES THE POWER WASTE.

IN THIS CASE:

- THE VOLTAGE DROP ACROSS BOTH LEDs IS NOW $3.2V + 3.2V = 6.4V$.
- THE REMAINING VOLTAGE ACROSS THE RESISTOR IS $9V - 6.4V = 2.6V$.
- USING OHM'S LAW AGAIN:

$$R = 2.6V / 0.02A = 130 \Omega \quad R = \frac{2.6V}{0.02A} = 130 \, \Omega$$

THE POWER DISSIPATED BY THE RESISTOR IS:

$$P = 2.6V \times 0.02A = 0.052W \quad P = 2.6V \times 0.02A = 0.052W$$

YOU'VE NOW SAVED POWER, AND YOU STILL GET THE SAME AMOUNT OF LIGHT FROM THE TWO LEDs!

ADVANCED LED HANDLING AND PROBLEMS

AT THIS POINT, YOU'RE LIKELY WONDERING: WHAT IF THE LED'S FORWARD VOLTAGE ISN'T EXACTLY **3.2V**? WHAT IF IT VARIES A LITTLE? THIS CAN BECOME PROBLEMATIC, ESPECIALLY WHEN YOU CONNECT MULTIPLE LEDs IN PARALLEL.

LED FORWARD VOLTAGE VARIATION

MANUFACTURERS USUALLY GIVE A TYPICAL FORWARD VOLTAGE (E.G., 3.2V), BUT IN PRACTICE, THE ACTUAL VOLTAGE CAN VARY SLIGHTLY BETWEEN INDIVIDUAL LEDs. IF YOU CONNECT LEDs IN PARALLEL WITH THE SAME RESISTOR, THE LEDs WITH LOWER FORWARD VOLTAGES WILL DRAW MORE CURRENT, CAUSING THEM TO BURN OUT FASTER. THE LEDs WITH HIGHER FORWARD VOLTAGES WILL BE UNDER-DRIVEN, PRODUCING LESS LIGHT.

THIS IS WHY THE VIDEO CREATOR CAUTIONS ABOUT USING ONE BIG RESISTOR FOR MULTIPLE LEDs IN PARALLEL. THE SOLUTION IS TO EITHER:

- **MEASURE THE CURRENT DIRECTLY AND ADJUST THE RESISTOR VALUES ACCORDINGLY.**
- **USE A CONSTANT CURRENT SOURCE INSTEAD OF A SIMPLE RESISTOR.**

USING A CONSTANT CURRENT SOURCE

THE BEST WAY TO DRIVE LEDs IS WITH A CONSTANT CURRENT RATHER THAN CONSTANT VOLTAGE. THIS ENSURES THAT EACH LED GETS EXACTLY THE CURRENT IT NEEDS, NO MATTER WHAT ITS INDIVIDUAL FORWARD VOLTAGE IS.

FOR EXAMPLE, YOU CAN USE AN LM317 VOLTAGE REGULATOR WITH A RESISTOR TO SET A CONSTANT CURRENT. THIS WORKS, BUT IT IS NOT VERY EFFICIENT. ANOTHER OPTION IS TO USE AN INTEGRATED CONSTANT CURRENT DRIVER LIKE THE TLZ 5940, WHICH IS MORE EFFICIENT BUT REQUIRES ADDITIONAL CIRCUITRY.

SUMMARY

- **RESISTORS ARE ESSENTIAL TO LIMIT CURRENT AND PREVENT LEDs FROM BURNING OUT.**
- **YOU CAN CALCULATE THE PROPER RESISTOR SIZE USING OHM'S LAW.**
- **FOR MULTIPLE LEDs, IT'S BETTER TO USE SERIES CONNECTIONS INSTEAD OF PARALLEL TO MINIMIZE POWER LOSS.**
- **WHEN DEALING WITH VARIATIONS IN LED FORWARD VOLTAGE, IT'S BETTER TO USE A CONSTANT CURRENT SOURCE.**

THIS VIDEO GIVES A THOROUGH OVERVIEW OF BOTH BEGINNER AND ADVANCED TECHNIQUES FOR PROPERLY USING LEDs. WHETHER YOU'RE JUST STARTING OUT OR HAVE EXPERIENCE, HANDLING LEDs WITH CARE ENSURES THEY WORK PROPERLY AND LAST LONGER.

PRO TIP: ALWAYS REMEMBER THAT EFFORT VERSUS BENEFIT IS A KEY FACTOR IN CHOOSING THE BEST METHOD FOR DRIVING LEDs. EVEN IF AN EASY SOLUTION WORKS, LIKE USING ONE RESISTOR FOR PARALLEL LEDs, IT'S NOT ALWAYS THE MOST EFFICIENT OR RELIABLE APPROACH IN THE LONG TERM.

55. USING A 7-SEGMENT DISPLAY FOR SIMPLE PROJECTS

IN THIS VIDEO, WE'LL EXPLORE HOW TO USE 7-SEGMENT DISPLAYS IN YOUR PROJECTS, BOTH WITH AND WITHOUT AN ARDUINO. THESE DISPLAYS MIGHT SEEM A BIT OLD-SCHOOL, BUT THEY'RE STILL INCREDIBLY USEFUL WHEN YOU NEED TO SHOW NUMBERS OR LETTERS FOR SIMPLE PROJECTS LIKE CLOCKS, TEMPERATURE SENSORS, OR POWER SUPPLIES.

TYPES OF 7-SEGMENT DISPLAYS

- **SINGLE-DIGIT:** A BASIC 7-SEGMENT DISPLAY WITH ONE DIGIT.
- **MULTI-DIGIT:** A MORE COMMON DISPLAY WITH MULTIPLE DIGITS IN ONE CASE (LIKE A 2-DIGIT DISPLAY).

NO MATTER WHICH DISPLAY YOU CHOOSE, ALWAYS CHECK THE DATASHEET FOR THE PINOUT. FOR EXAMPLE, I'M USING THE **LTS-546** DISPLAY, WHICH IS A COMMON TYPE FOR SMALL PROJECTS. THE DATASHEET TELLS US THAT THE DISPLAY HAS **8 INDIVIDUAL LEDs** (7 SEGMENTS PLUS 1 DECIMAL POINT) AND IS COMMON ANODE. THIS MEANS THAT ALL THE LEDs SHARE A COMMON POSITIVE PIN (EITHER PIN 3 OR PIN 8), AND EACH SEGMENT IS CONTROLLED BY AN INDIVIDUAL PIN FOR THE CATHODE (NEGATIVE SIDE).

KEY PINS ON THE DISPLAY:

- **SEGMENTS:** A TO G (REPRESENTING THE 7 SEGMENTS OF EACH DIGIT)
- **DECIMAL POINT:** DP (FOR THE DECIMAL POINT)
- **COMMON ANODE:** PIN 3 OR PIN 8 (COMMON POSITIVE TERMINAL)

DISPLAYING NUMBERS WITHOUT AN ARDUINO

TO DRIVE THE DISPLAY WITHOUT AN ARDUINO, YOU CAN USE A **BCD TO 7-SEGMENT DISPLAY DRIVER IC**. IN THIS CASE, I'M USING THE **SN7447 IC**. THIS DRIVER CAN CONVERT BINARY CODED DECIMAL (**BCD**) INPUT INTO SIGNALS THAT LIGHT UP THE CORRECT SEGMENTS FOR EACH NUMBER.

THE IC HAS ACTIVE-LOW INPUTS, MEANING THE SEGMENTS ARE ACTIVATED BY A LOW SIGNAL. YOU'LL NEED TO CONNECT THE DISPLAY TO THE IC, WITH RESISTORS (TYPICALLY **220Ω**) TO LIMIT THE CURRENT AND PROTECT THE LEDs. HERE'S HOW IT WORKS:

1. **CONNECT THE BCD INPUTS (A, B, C, D) TO CONTROL THE DISPLAYED DIGIT.**
2. **USE THE LAMP TEST PIN TO CHECK THAT ALL SEGMENTS LIGHT UP CORRECTLY WHEN GROUNDED.**

3. THE COMBINATION OF INPUTS WILL DETERMINE WHICH DIGIT APPEARS ON THE DISPLAY . FOR EXAMPLE, A COMBINATION OF LOW ON **A**, HIGH ON **B**, AND LOW ON **C** WILL DISPLAY THE NUMBER 6.

CONTROLLING THE INPUTS WITHOUT A MICROCONTROLLER:

TO CONTROL THE INPUTS WITHOUT AN ARDUINO, WE CAN USE A 4-BIT BINARY COUNTER LIKE THE **SN7490**. THIS COUNTER WILL INCREMENT THE NUMBER DISPLAYED ON THE 7-SEGMENT DISPLAY, MAKING IT A SIMPLE SOLUTION TO COUNT NUMBERS MANUALLY.

- CONNECT THE COUNTER'S OUTPUT PINS TO THE **BCD** INPUTS ON THE DISPLAY DRIVER IC.
- USE A PUSH-BUTTON TO TRIGGER THE COUNT, OR CONNECT A SENSOR TO INCREMENT THE COUNT (E.G., A TILT SWITCH OR INFRARED SENSOR).

USING MULTIPLE DIGITS

IF YOU NEED MORE THAN ONE DIGIT, LIKE A CLOCK, YOU'LL RUN INTO THE ISSUE OF NEEDING TO CONTROL MULTIPLE DIGITS AT THE SAME TIME. FOR EXAMPLE, A 16-LED DISPLAY WITH 2 COMMON ANODES FOR THE LEFT AND RIGHT DIGITS REQUIRES MORE PINS TO CONTROL. BUT DON'T WORRY — MULTIPLEXING IS THE SOLUTION.

MULTIPLEXING

MULTIPLEXING ALLOWS YOU TO CONTROL MULTIPLE DIGITS WITH FEWER PINS BY RAPIDLY SWITCHING BETWEEN THEM. BY SWITCHING BETWEEN THE DIGITS VERY QUICKLY, YOUR EYES PERCEIVE THEM AS BEING ON AT THE SAME TIME. FOR THIS, WE ONLY NEED 12 PINS:

- 8 PINS FOR THE SEGMENTS (**A** TO **G**)
- 4 PINS FOR THE COMMON ANODES

TO CONTROL THE MULTIPLEXING, WE CAN USE A SPECIALIZED IC: THE **SI1064**. THIS IC IS DESIGNED TO HANDLE MULTIPLEXED 7-SEGMENT DISPLAYS AND CAN CONTROL UP TO 4 DIGITS USING THE **I2C** COMMUNICATION PROTOCOL. THE **I2C** PROTOCOL ALLOWS FOR MORE EFFICIENT USE OF THE ARDUINO'S PROCESSING POWER, ESPECIALLY IF YOU'RE WORKING WITH MULTIPLE DIGITS.

CIRCUIT FOR MULTIPLEXING WITH **SI1064**:

1. **I2C COMMUNICATION:** WE CONNECT THE **SI1064** IC TO THE ARDUINO USING **I2C** (PINS **A4** FOR **SDA** AND **A5** FOR **SCL**).
2. **TRANSISTORS FOR MULTIPLEXING:** TWO BASIC **NPN** TRANSISTORS (LIKE THE **BC337**) ARE USED TO SWITCH BETWEEN THE COMMON ANODES OF THE LEFT AND RIGHT DIGITS.

3. CAPACITORS AND RESISTORS: USE A 2.2nF CAPACITOR FOR SPEED CONTROL AND PULL-UP RESISTORS (4.7kΩ) TO STABILIZE THE I2C COMMUNICATION.

ONCE THE CIRCUIT IS SET UP, UPLOAD THE I2C LIBRARY CODE TO THE ARDUINO, AND YOU'LL HAVE A WORKING 4-DIGIT DISPLAY WITH MINIMAL PROCESSING POWER REQUIRED.

CODE FOR I2C COMMUNICATION

TO INTERACT WITH THE SI1064 AND CONTROL THE DISPLAY, YOU'LL NEED A LIBRARY THAT SIMPLIFIES I2C COMMUNICATION. FORTUNATELY, THERE ARE LIBRARIES AVAILABLE THAT LET YOU CONTROL THE DISPLAY WITH JUST A FEW COMMANDS. BY USING THE LIBRARY, YOU CAN EASILY DISPLAY NUMBERS, TEXT, OR EVEN CREATE A CLOCK WITHOUT OVERLOADING THE ARDUINO'S PROCESSING CAPABILITIES.

CONCLUSION

- **7-SEGMENT DISPLAYS ARE A SIMPLE AND EFFECTIVE WAY TO DISPLAY NUMBERS OR LETTERS IN PROJECTS.**
- **FOR BASIC USE, A BCD TO 7-SEGMENT DRIVER IC LIKE THE SN7447 WILL ALLOW YOU TO CONTROL THE DISPLAY WITHOUT A MICROCONTROLLER.**
- **FOR MULTIPLE DIGITS, YOU CAN USE MULTIPLEXING AND A SPECIALIZED IC LIKE THE SI1064 TO MANAGE THE DISPLAY WITH I2C COMMUNICATION, SAVING ARDUINO RESOURCES.**
- **I2C AND MULTIPLEXING MAKE MANAGING MULTI-DIGIT DISPLAYS MUCH EASIER AND MORE EFFICIENT.**

THIS APPROACH TO 7-SEGMENT DISPLAYS CAN BE USED FOR CLOCKS, COUNTERS, POWER SUPPLIES, AND MANY OTHER PROJECTS. EXPERIMENT WITH THE WIRING AND LIBRARIES TO EXPLORE MORE ADVANCED POSSIBILITIES!

PRO TIP: WHEN DEALING WITH I2C, MAKE SURE TO CHECK OUT DETAILED TUTORIALS (LIKE TRONIC STAFF'S) TO FULLY UNDERSTAND THE COMMUNICATION PROTOCOL AND HOW TO USE IT EFFECTIVELY.

56. HOW TO BUILD YOUR OWN ARDUINO ON A BREADBOARD AND EMBED IT IN A PROJECT

IN TODAY'S VIDEO, I'LL SHOW YOU HOW TO BREAK YOUR ATMEGA328P MICROCONTROLLER FREE FROM THE ARDUINO UNO AND EMBED IT DIRECTLY INTO YOUR PROJECT. THIS IS A GREAT SOLUTION IF YOU WANT TO MAKE A MORE COMPACT DESIGN AND USE YOUR ARDUINO UNO'S RESOURCES FOR OTHER THINGS.

STEP 1: TEST YOUR CIRCUIT ON A BREADBOARD

BEFORE JUMPING INTO THE ACTUAL EMBEDDING PROCESS, IT'S ALWAYS A GOOD IDEA TO TEST YOUR CIRCUIT ON A BREADBOARD. ONCE EVERYTHING WORKS FINE ON THE BREADBOARD, WE CAN MOVE ON TO TRANSFERRING IT TO A PCB OR EMBEDDING IT INTO A PROJECT.

FOR THE ATMEGA328P MICROCONTROLLER, YOU'LL NEED JUST A FEW COMPONENTS TO MAKE IT WORK:

- **16 MHz CLOCK CRYSTAL**
- **TWO 22 pF CAPACITORS (TO STABILIZE THE CLOCK)**
- **10kΩ RESISTOR (TO PREVENT THE MICROCONTROLLER FROM RESETTING ITSELF)**

STEP 2: WIRING THE ATMEGA328P MICROCONTROLLER

THE WIRING FOR THE ATMEGA328P IS SIMILAR TO WHAT YOU'D FIND ON A REGULAR ARDUINO UNO, BUT WITH A FEW KEY DIFFERENCES.

HERE'S A QUICK BREAKDOWN:

- **CLOCK: THE 16 MHz CRYSTAL CONNECTS TO PINS 9 AND 10 OF THE ATMEGA328P, WITH A 22 pF CAPACITOR CONNECTING EACH PIN TO GROUND.**
- **RESET PIN: THE 10kΩ RESISTOR CONNECTS FROM THE RESET PIN TO 5V, PREVENTING THE MICROCONTROLLER FROM RESETTING UNNECESSARILY.**
- **POWER: PINS 7, 20, AND 21 CONNECT TO 5V, WHILE PINS 8 AND 22 CONNECT TO GROUND.**

THIS IS ESSENTIALLY A BREADBOARD VERSION OF THE ARDUINO UNO. KEEP IN MIND, THIS SETUP DOESN'T COME WITH SOME OF THE CONVENIENT FEATURES OF A REGULAR ARDUINO, SUCH AS:

- **NO RESET SWITCH**
- **NO BUILT-IN USB-TO-SERIAL CONVERSION**
- **NO OVER-VOLTAGE OR SHORT-CIRCUIT PROTECTION**

BUT IF YOU'RE COMFORTABLE WITH BASIC ELECTRONICS, THESE OMISSIONS CAN BE WORKED AROUND.

STEP 3: PINOUT MAPPING

HERE'S THE CRUCIAL PART: MAPPING THE ARDUINO PINS TO THE ATMEGA328P'S PINS. THE ATMEGA328P USES DIFFERENT PIN NUMBERS THAN THE ARDUINO UNO, SO YOU'LL NEED TO

REFER TO THE PINOUT FOR CORRECT MAPPING. FOR EXAMPLE, IF YOU'RE USING DIGITAL PIN 9 ON THE ARDUINO, IT SHOULD BE CONNECTED TO PIN 15 ON THE ATMEGA328P, AND SO ON.

STEP 4: UPLOADING YOUR CODE

THERE ARE SEVERAL WAYS TO UPLOAD CODE TO THE ATMEGA328P ONCE IT'S ON THE BREADBOARD:

- 1. THE LAZIEST (BUT MOST ANNOYING) WAY: REMOVE THE ATMEGA328P FROM THE BREADBOARD AND PLUG IT INTO AN ARDUINO UNO TO UPLOAD YOUR CODE.**
- 2. USING THE ARDUINO'S SERIAL PINS:**
 - **CONNECT THE TX PIN OF YOUR ARDUINO TO PIN 3 (Rx) OF THE ATMEGA328P.**
 - **CONNECT THE RX PIN OF YOUR ARDUINO TO PIN 2 (Tx) OF THE ATMEGA328P.**
 - **CONNECT THE RESET PIN OF YOUR ARDUINO TO PIN 1 OF THE ATMEGA328P.**

THIS WAY, YOU CAN UPLOAD CODE JUST LIKE YOU WOULD NORMALLY DO WITH THE ARDUINO UNO.

- 3. USING AN FTDI USB-TO-SERIAL ADAPTER:**

- **IF YOU DON'T WANT TO USE THE ARDUINO UNO TO UPLOAD CODE, YOU CAN USE AN FTDI CHIP (USB-TO-SERIAL ADAPTER).**
- **CONNECT RX TO TX, TX TO RX, AND RESET TO RESET.**
- **THIS GIVES YOU USB-TO-SERIAL FUNCTIONALITY AND ALLOWS YOU TO UPLOAD YOUR SKETCHES THROUGH THE ARDUINO IDE.**

- 4. IN-CIRCUIT SERIAL PROGRAMMING (ICSP):**

- **THIS IS A MORE ADVANCED METHOD WHERE YOU CAN PROGRAM THE ATMEGA328P DIRECTLY USING A SPECIAL PROGRAMMER AND SEPARATE SOFTWARE. BUT THIS IS GENERALLY MORE COMPLEX, SO IT'S RECOMMENDED FOR THOSE WHO ARE ALREADY EXPERIENCED.**

STEP 5: EMBEDDING THE ATMEGA328P IN A PROJECT

ONCE EVERYTHING IS WORKING ON THE BREADBOARD AND YOU'RE CONFIDENT THAT THE CIRCUIT IS FUNCTIONING CORRECTLY, YOU CAN PROCEED TO SOLDER THE COMPONENTS ONTO A PCB (PRINTED CIRCUIT BOARD). MAKE SURE TO LEAVE SPACE FOR THE RX AND TX HEADERS IN CASE YOU NEED TO REPROGRAM THE MICROCONTROLLER LATER.

THIS IS A GREAT WAY TO CREATE A COMPACT, STANDALONE ARDUINO-BASED PROJECT WITHOUT NEEDING THE FULL ARDUINO UNO BOARD.

57. CONTROLLING A LARGE LED MATRIX WITH ARDUINO NANO

- **PROBLEM: CONTROLLING A LARGE NUMBER OF LEDs (E.G., 50 IN A MATRIX OR 192 IN A CUBE) EXCEEDS THE I/O PINS AVAILABLE ON A TYPICAL MICROCONTROLLER, EVEN AN ARDUINO MEGA.**
- **SOLUTION: USE AN ARDUINO NANO, TLC5940 LED DRIVER, AND P-CHANNEL MOSFETS TO CONTROL MULTIPLE LEDs WITH FEWER I/O PINS.**
- **STEPS:**
 1. **LED WIRING: CONNECT CATHODES (NEGATIVE PINS) OF LEDs TO COLUMNS AND ANODES (POSITIVE PINS) TO ROWS.**
 2. **MULTIPLEXING: LIGHT UP ONE ROW AT A TIME RAPIDLY TO GIVE THE ILLUSION OF ALL LEDs BEING LIT SIMULTANEOUSLY.**
 3. **MOSFETS: USE P-CHANNEL MOSFETS TO SWITCH THE ANODE ROWS ON/OFF AND REDUCE CURRENT DRAW.**
 4. **TLC5940 DRIVER: USE THE TLC5940 FOR CONTROLLING THE CATHODE COLUMNS WITH 10 OUTPUTS.**
 5. **RESISTORS: USE 1K RESISTORS FOR MOSFET PULL-UPS AND A 2K RESISTOR TO SET CONSTANT CURRENT FOR THE TLC5940.**
- **CODE: USE THE TLC5940 LIBRARY FOR EASY CONTROL OF THE LEDs.**
- **RESULT: A WORKING LED MATRIX OR CUBE CONTROLLED BY A FEW I/O PINS, MAKING IT EFFICIENT TO CONTROL MANY LEDs WITHOUT USING ALL MICROCONTROLLER PINS.**

58. CONTROLLING LEDs WITH BLUETOOTH AND ARDUINO NANO

- **GOAL: USE A BLUETOOTH MODULE (HC-05) WITH AN ARDUINO NANO TO CONTROL AN RGB LED USING AN ANDROID APP.**

- **BLUETOOTH MODULE:** THE **HC-05** MODULE OPERATES AT **3.3V** LOGIC LEVELS, WHILE THE **ARDUINO** USES **5V**. USE A VOLTAGE DIVIDER (**2kΩ** AND **4.7kΩ** RESISTORS) TO SAFELY CONNECT THE **TX** PIN OF THE **ARDUINO** TO THE **RX** PIN OF THE **BLUETOOTH** MODULE.
- **LED WIRING:** CONNECT A COMMON ANODE **RGB LED** TO THE **ARDUINO NANO**. EACH CATHODE (**RGB**) GOES THROUGH A **460-OHM** RESISTOR TO DIGITAL PINS **8, 9, AND 10**.
- **APP:** USE THE **S2 TERMINAL** APP (FREE, AVAILABLE ON THE **PLAY STORE**) TO SEND COMMANDS LIKE "RED," "GREEN," OR "BLUE" TO THE **ARDUINO** VIA **BLUETOOTH**.
- **ARDUINO CODE:** PROGRAM THE **ARDUINO** TO RESPOND TO **ASCII** TEXT (E.G., "RED" TO TURN THE **LED** RED). REMEMBER TO DISCONNECT THE **BLUETOOTH TX/RX** WHEN UPLOADING CODE TO AVOID INTERFERENCE.
- **OUTCOME:** PAIR THE **BLUETOOTH** MODULE WITH THE PHONE (DEFAULT PAIRING CODE: **1234** OR **0000**) AND CONTROL THE **RGB LED** VIA SIMPLE TEXT COMMANDS.

59. USING **ATTINY 85** WITH **WS2801 LED STRIP** AND A **BUTTON**

- **GOAL:** CONTROL **WS2801 LED STRIP** ANIMATIONS WITH A **BUTTON**, USING AN **ATTINY 85** MICROCONTROLLER TO SAVE RESOURCES.
- **WHY ATTINY 85:** THE **ATTINY 85** IS AN AFFORDABLE ALTERNATIVE TO THE **ATMEGA328**, WITH **5 I/Os** AND **8KB** FLASH MEMORY, PERFECT FOR SIMPLE **LED** CONTROL.
- **SETUP:**
 - **ARDUINO AS PROGRAMMER:** USE AN **ARDUINO UNO** AS A PROGRAMMER TO UPLOAD CODE TO THE **ATTINY 85**.
 - **INSTALL ATTINY LIBRARIES:** DOWNLOAD AND INSTALL THE **ATTINY CORE** FROM **HIGHLOWTECH.ORG** AND ADD IT TO THE **ARDUINO IDE**.
 - **WIRING:** CONNECT THE **ARDUINO UNO** TO THE **ATTINY 85** FOLLOWING THE PINOUT. USE A **10μF** CAPACITOR BETWEEN THE **RESET** PIN OF **ARDUINO** AND **GROUND**.
- **PROGRAMMING:**
 - **UPLOAD ARDUINO ISP SKETCH:** LOAD THE **ARDUINO ISP** SKETCH TO THE **UNO** FOR PROGRAMMING THE **ATTINY**.
 - **WRITE CODE:** UPLOAD A SIMPLE **BLINK** SKETCH TO TEST THE SETUP. USE **IO** PINS FOR CONTROLLING THE **LED STRIP** (USING **IO 3** FOR THE TEST).

- **ENHANCEMENT:**
 - **CREATE AN ATTINY PROGRAMMING SHIELD TO AVOID WIRING EACH TIME. USE MALE HEADERS, AN IC SOCKET, AND A PCB.**
- **LIMITATIONS:**
 - **ATTINY DOESN'T SUPPORT ALL ARDUINO FUNCTIONS (E.G., SPI FOR WS2801), BUT BIT-BANGING (EMULATING SPI) CAN BE USED FOR CONTROL.**
- **NEXT STEPS: FURTHER DEVELOP THE PROJECT TO CONTROL WS2801 LEDs WITH THE ATTINY 85.**

60. PWM DIMMING FOR LEDs

- **WHAT IS PWM?**
 - **PWM (PULSE WIDTH MODULATION) IS A TECHNIQUE FOR CONTROLLING THE BRIGHTNESS OF LEDs BY SWITCHING THE LED ON AND OFF RAPIDLY. THE "DUTY CYCLE" CONTROLS THE BRIGHTNESS:**
 - **100% DUTY CYCLE: LED IS FULLY ON.**
 - **50% DUTY CYCLE: LED IS ON FOR HALF THE TIME, DIMMER.**
 - **20% DUTY CYCLE: LED IS DIMMER, REPRESENTING LOWER VOLTAGE (AROUND 1V).**
- **WHY NOT JUST USE A POTENTIOMETER?**
 - **A POTENTIOMETER IN SERIES WITH THE LED CAN DIM IT, BUT IT WASTES ENERGY (HEATS UP) AND REQUIRES A ROBUST ONE FOR HIGH-POWER LEDs, WHICH IS INEFFICIENT.**
- **PWM WITH AN ARDUINO:**
 - **USE ANALOGWRITE() ON PWM-CAPABLE PINS (LIKE PIN 3) TO CREATE A SIGNAL THAT TURNS THE LED ON AND OFF RAPIDLY.**
 - **THE VALUE FED INTO ANALOGWRITE() (BETWEEN 0 AND 255) CONTROLS THE DUTY CYCLE:**
 - **0 = 0V (OFF), 255 = 5V (FULLY ON).**
- **PWM WITHOUT AN ARDUINO:**

- YOU CAN USE A **555** TIMER IC TO CREATE **PWM** SIGNALS WITHOUT A MICROCONTROLLER. A POTENTIOMETER ADJUSTS THE DUTY CYCLE.
- FOR HIGHER POWER, USE A **MOSFET** TO CONTROL THE **LED** STRIP BY CONNECTING THE **PWM** SIGNAL TO THE GATE.
- **PRACTICAL APPLICATION:**
 - **BENCH POWER SUPPLY:** IF YOU LOWER THE VOLTAGE BELOW THE **LED'S** FORWARD VOLTAGE, IT DIMS, BUT **PWM** DOES IT MORE EFFICIENTLY.
 - **WITH MOSFETS,** YOU CAN HANDLE HIGHER CURRENT AND VOLTAGE, ESPECIALLY FOR **LED STRIPS** OR HIGH-POWER **LEDs**.

61. USING A BASIC MULTIMETER

- **OHM'S LAW: MULTIMETERS CAN MEASURE VOLTAGE, CURRENT, AND RESISTANCE BASED ON OHM'S LAW:**
 - **RESISTANCE (R) = VOLTAGE (V) / CURRENT (I)**
 - **VOLTAGE (V) = RESISTANCE (R) × CURRENT (I)**
 - **CURRENT (I) = VOLTAGE (V) / RESISTANCE (R)**
- **MEASURING RESISTANCE:**
 - **SET THE MULTIMETER TO THE OHM SIGN (Ω).**
 - **CONNECT THE PROBES TO BOTH ENDS OF THE RESISTOR.**
 - **NOTE: MEASURING RESISTANCE IN A LIVE CIRCUIT MIGHT GIVE INCORRECT RESULTS, AS CURRENT WILL FIND THE PATH OF LEAST RESISTANCE.**
- **CONTINUITY TEST:**
 - **SWITCH TO THE CONTINUITY MODE (A BEEPING SYMBOL).**
 - **THE MULTIMETER WILL BEEP IF THERE'S ALMOST ZERO RESISTANCE, USEFUL FOR CHECKING FOR BROKEN WIRES.**
- **MEASURING VOLTAGE:**
 - **TO MEASURE DC VOLTAGE (MOST COMMON), SET THE MULTIMETER TO DC VOLTAGE MODE (V WITH A STRAIGHT LINE).**

- **CONNECT THE RED PROBE TO THE POSITIVE TERMINAL AND THE BLACK PROBE TO THE NEGATIVE TERMINAL.**
- ***EXAMPLE:* CHECK IF A BATTERY OR POWER SUPPLY IS WORKING CORRECTLY BY MEASURING ITS VOLTAGE.**
- **MEASURING CURRENT:**
 - **SWITCH THE RED PROBE TO THE 10A SOCKET FOR HIGH CURRENT (UP TO 10A).**
 - **TO MEASURE CURRENT, BREAK THE CIRCUIT AND PLACE THE MULTIMETER IN SERIES.**
 - ***TIP:* START WITH THE HIGHEST CURRENT RANGE TO PREVENT BLOWING THE FUSE (USUALLY 500mA MAX IN THE LOW-CURRENT SOCKET).**
- **FIXING FUSE ISSUES:**
 - **IF THE MULTIMETER DOESN'T MEASURE CURRENT, THE FUSE MIGHT BE BLOWN.**
 - **OPEN THE MULTIMETER, REPLACE THE FUSE WITH ONE OF THE SAME VALUE, AND REASSEMBLE.**